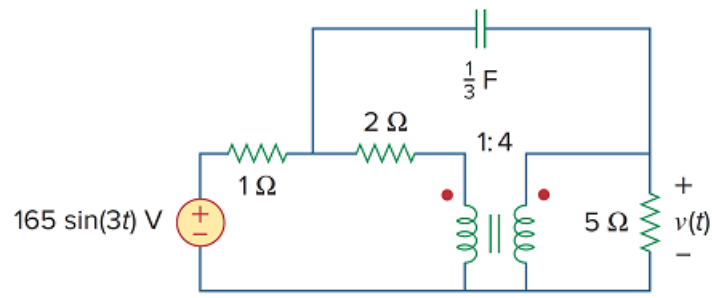


Problem

Find $v(t)$ for the circuit in Fig. 13.112.

Figure 13.112



Step-by-step solution

Step 1 of 5

Refer to Figure 13.112 in the textbook.

The expression for the input voltage source is,

$$\begin{aligned} v_s(t) &= 165 \sin(3t) \\ &= 165 \cos(3t - 90^\circ) \end{aligned}$$

The phasor values are,

$$\mathbf{V}_s = 165 \angle -90^\circ \text{ V}$$

$$\omega = 3 \text{ rad/s}$$

The impedance of capacitor is,

$$\begin{aligned} \mathbf{Z}_C &= \frac{1}{j\omega C} \\ &= \frac{1}{j(3)\left(\frac{1}{3}\right)} \\ &= -j \Omega \end{aligned}$$

Step 2 of 5

Draw the circuit in frequency domain.

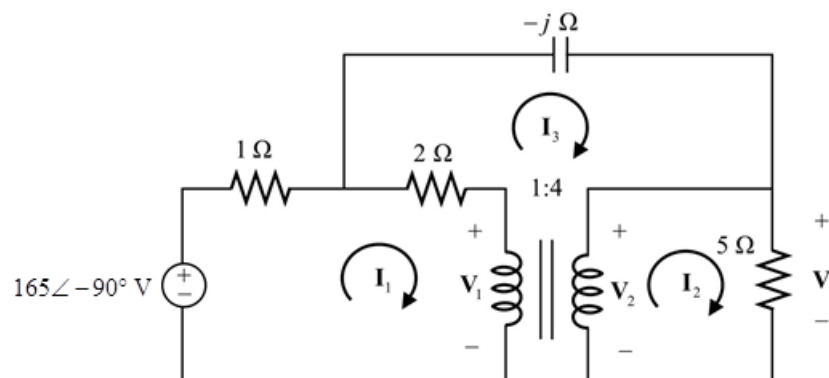


Figure 1

From Figure 1,

$$\begin{aligned} V_2 &= V \\ &= 5I_2 \end{aligned}$$

Calculate the primary and secondary voltage relation.

$$\begin{aligned} \frac{V_1}{V_2} &= \frac{N_1}{N_2} \\ \frac{V_1}{5I_2} &= \frac{1}{4} \\ V_1 &= \frac{5I_2}{4} \\ V_1 &= 1.25I_2 \end{aligned}$$

Step 4 of 5

Calculate the primary and secondary current relation.

$$\begin{aligned} \frac{I_1}{I_2} &= \frac{N_2}{N_1} \\ \frac{I_1}{I_2} &= \frac{4}{1} \\ I_1 &= 4I_2 \end{aligned}$$

Apply Kirchhoff's voltage law to loop1.

$$\begin{aligned} -165\angle -90^\circ + (1)I_1 + (2)(I_1 - I_3) + V_1 &= 0 \\ 3I_1 - 2I_3 + V_1 &= 165\angle -90^\circ \end{aligned}$$

Substitute $1.25I_2$ for V_1 and $4I_2$ for I_1 .

$$\begin{aligned} 3(4I_2) - 2I_3 + 1.25I_2 &= 165\angle -90^\circ \\ 13.25I_2 - 2I_3 &= 165\angle -90^\circ \\ 2I_3 &= 13.25I_2 - 165\angle -90^\circ \\ I_3 &= 6.625I_2 - 82.5\angle -90^\circ \end{aligned}$$

Apply Kirchhoff's voltage law to outer loop.

$$\begin{aligned} (-j)I_3 + V_2 - 165\angle -90^\circ + (1)I_1 &= 0 \\ (-j)I_3 + I_1 + V_2 &= 165\angle -90^\circ \end{aligned}$$

Substitute $6.625I_2 - 82.5\angle -90^\circ$ for I_3 , $5I_2$ for V_2 and $4I_2$ for I_1 .

$$\begin{aligned} (-j)(6.625I_2 - 82.5\angle -90^\circ) + 4I_2 + 5I_2 &= 165\angle -90^\circ \\ (-j)(6.625I_2 + 82.5j) + 4I_2 + 5I_2 &= -165j \\ (-j6.625)I_2 + 82.5 + 9I_2 &= -165j \\ (9 - j6.625)I_2 &= -82.5 - j165 \\ I_2 &= \frac{-82.5 - j165}{9 - j6.625} \\ &= 2.8075 - j16.2667 \\ &= 16.5072\angle -80.2077^\circ \text{ A} \end{aligned}$$

[Comments \(1\)](#)



Anonymous

why does the KVL for loop 3 include the voltage source?

Calculate the output voltage, $\mathbf{V}$.

$$\begin{aligned}\mathbf{V} &= \mathbf{V}_2 \\ &= 5\mathbf{I}_2 \\ &= 5(16.5072\angle -80.2077^\circ) \\ &= 82.536\angle -80.2077^\circ \text{ V}\end{aligned}$$

Convert the output voltage in phasor domain to time domain.

$$v(t) = 82.536 \cos(3t - 80.2077^\circ) \text{ V}$$

Thus, the output voltage is $\boxed{82.536 \cos(3t - 80.2077^\circ) \text{ V}}$.