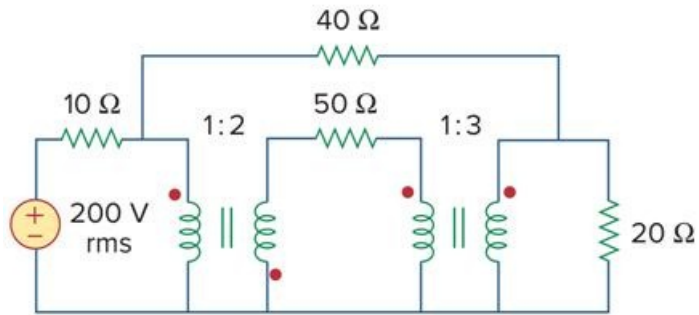


Problem

Calculate the average power dissipated by the $20\text{-}\Omega$ resistor in Fig. 13.130.

Figure 13.130



Step-by-step solution

Step 1 of 5

Refer to Figure 13.129 in the textbook.

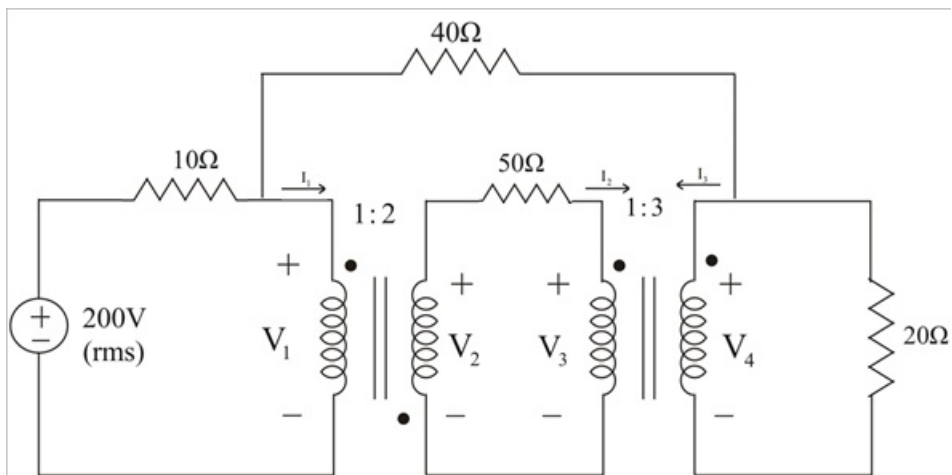


Figure 1

Step 2 of 5

Apply Kirchhoff's current law at node 1.

$$\frac{200 - V_1}{10} = \frac{V_1 - V_4}{40} + I_1$$

$$4(200 - V_1) = V_1 - V_4 + 40I_1$$

$$5V_1 - V_4 + 40I_1 = 800 \quad \dots\dots (1)$$

Apply Kirchhoff's current law at node 2.

$$\frac{V_1 - V_4}{40} = \frac{V_4}{20} + I_3$$

$$V_1 = 3V_4 + 40I_3 \quad \dots\dots (2)$$

Calculate the ratio of primary voltage to secondary voltage of first transformer.

$$\begin{aligned} \frac{V_2}{V_1} &= -\frac{N_2}{N_1} \\ &= -2 \end{aligned}$$

$$V_2 = -2V_1 \quad \dots\dots (3)$$

$$\begin{aligned} \frac{I_2}{I_1} &= -\frac{N_1}{N_2} \\ &= -\frac{1}{2} \end{aligned}$$

$$I_1 = -2I_2 \quad \dots\dots (4)$$

Apply Kirchhoff's voltage law for the middle loop.

$$-V_2 + 50I_2 + V_3 = 0$$

$$V_3 = V_2 - 50I_2 \quad \dots\dots (5)$$

Step 3 of 5

Calculate the ratio of currents and voltages at the terminals of second transformer.

$$\begin{aligned} \frac{V_4}{V_3} &= \frac{N_2}{N_1} \\ &= 3 \end{aligned}$$

$$V_4 = 3V_3 \quad \dots\dots (6)$$

$$\begin{aligned} \frac{I_3}{I_2} &= -\frac{N_1}{N_2} \\ &= -\frac{1}{3} \end{aligned}$$

$$I_2 = -3I_3 \quad \dots\dots (7)$$

Step 4 of 5

From equations (1) and (2),

$$14V_4 + 200I_3 + 40I_1 = 800$$

Substitute $3I_3$ for I_2 in equation (4).

$$\begin{aligned} I_1 &= -2I_2 \\ &= -2(3I_3) \\ &= -6I_3 \end{aligned}$$

$$14V_4 + 200I_3 + 40(-6I_3) = 800$$

$$14V_4 - 40I_3 = 800$$

$$V_3 = V_2 - 50I_2$$

$$\begin{aligned} V_4 &= 3(V_2 - 50I_2) \\ &= 3V_2 - 150I_2 \\ &= 3(-2V_1) - 150(-3I_3) \end{aligned}$$

$$\begin{aligned} V_4 &= -6V_1 + 450I_3 \\ &= -6(3V_4 + 40I_3) + 450I_3 \\ &= -18V_4 + 210I_3 \end{aligned}$$

$$19V_4 = 210I_3$$

$$I_3 = \frac{19}{210}V_4$$

Substitute $\frac{19}{210}V_4$ for I_3 in equation (1).

$$200 = 13.452V_4$$

$$V_4 = 14.87$$

Step 5 of 5

The average power dissipated by the $20\ \Omega$ resistor is,

$$\begin{aligned} P_{20\ \Omega} &= \frac{V_4^2}{20} \\ &= \frac{14.87^2}{20} \\ &= 11.05\ \text{W} \end{aligned}$$

The average power dissipated by the $20\ \Omega$ resistor is 11.05 W.