

Problem

In order to meet an emergency, three single-phase transformers with 12,470/7,200 V rms are connected in Δ -Y to form a three-phase transformer which is fed by a 12,470-V transmission line. If the transformer supplies 60 MVA to a load, find:

(a) the turns ratio for each transformer,

(b) the currents in the primary and secondary windings of the transformer,


(c) the incoming and outgoing transmission line currents.

Step-by-step solution

Step 1 of 5

(A) Consider just one phase at a time,

Step 2 of 5

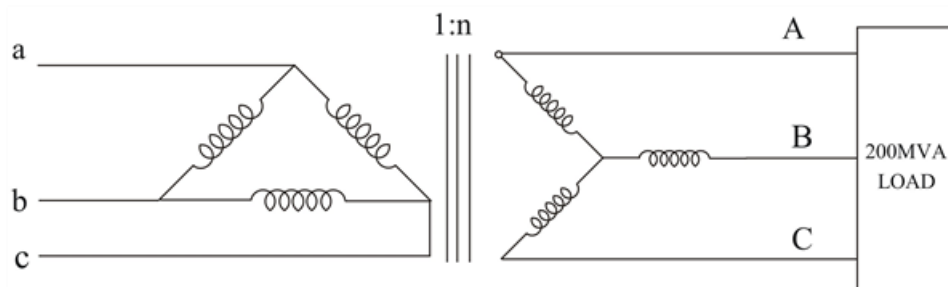

Step 3 of 5

$$n = \frac{V_L}{\sqrt{3}V_{LP}} = \frac{7200}{(12470\sqrt{3})} = \frac{1}{3}.$$

Step 4 of 5

(B) The load carried by each transformer is,

$$\frac{60}{3} = 20 \text{ MVA}$$

Hence,

$$I_{LP} = \frac{20 \text{ MVA}}{12.47 \text{ K}} = 1604 \text{ A}$$

$$I_{LS} = \frac{20 \text{ MVA}}{7.2 \text{ K}} = 2778 \text{ A}.$$

Step 5 of 5

(C) The current in incoming line is A, B, C is,

$$\sqrt{3} LP = \sqrt{3} \times 1603.85 = 2778 A$$

Current in each outgoing line A, B, C is,

$$\frac{2778}{(n\sqrt{3})} = 4812 A .$$