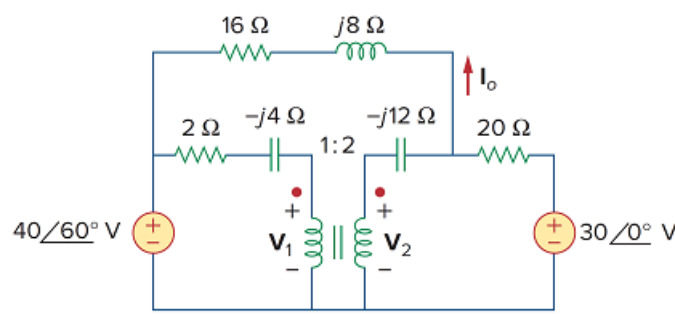


Problem

Use *PSpice* or *MultiSim* to find V_1 , V_2 , and I_o in the circuit of Fig. 13.143.

Figure 13.143



Step-by-step solution

Step 1 of 2

The schematic is shown below. In the AC sweep box, we type pts = 1, start frequency = 0.1592, and end frequency = 0.1592. After simulation, we obtain the output file which includes,

Frequency	1 M(V_Print1)	1 P(V_Print1)
1.592 E-01	1.955 E+01	8.332 E+01
Frequency	1 M(V_Print2)	1 P(V_Print2)
1.592 E-01	6.847 E+01	4.640 E+01
Frequency	1 M(V_Print1)	1 P(V_Print1)
1.592 E-01	4.340 E-01	-9.260 E+01

i.e.,

$$V_1 = 19.55 \angle 83.32^\circ \text{ V}$$

$$V_2 = 68.47 \angle 46.4^\circ \text{ V}$$

$$I_o = 443.4 \angle -92.6^\circ \text{ mA}$$

Step 2 of 2

