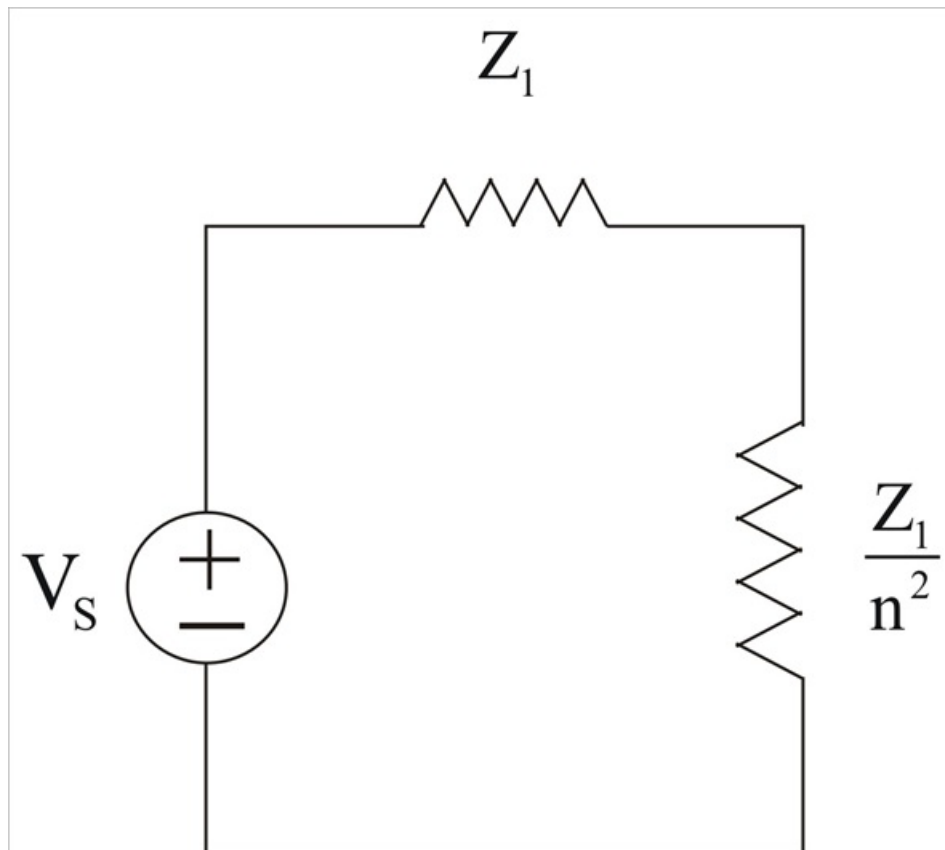


## Problem

A stereo amplifier circuit with an output impedance of  $7.2\text{ k}\Omega$  is to be matched to a speaker with an input impedance of  $8\text{ }\Omega$  by a transformer whose primary side has 3,000 turns. Calculate the number of turns required on the secondary side.

## Step-by-step solution

## Step 1 of 2



## Step 2 of 2

For maximum power transfer,

$$Z_1 = \frac{Z_L}{n^2}$$

$$\Rightarrow n^2 = \frac{Z_L}{Z_1} = \frac{8}{7200}$$

$$n^2 = \frac{1}{900}$$

$$n = \frac{1}{30} = \frac{N_2}{N_1}$$

Thus,

$$N_2 = \frac{N_1}{30} = \frac{3000}{30}$$

$$= 100 \text{ Turns} .$$