

Problem

A 440/110-V ideal transformer can be connected to become a 550/440-V ideal autotransformer. There are four possible connections, two of which are wrong. Find the output voltage of:

(a) a wrong connection,

(b) the right connection.

Step-by-step solution


Step 1 of 5



$$\frac{V_2}{V_1} = \frac{110}{440}$$



$$= \frac{1}{4} = \frac{I_1}{I_2}$$

There are four ways of hooking up the transformer as an auto – transformer; however it is clear that there are only two outcomes.

Step 2 of 5

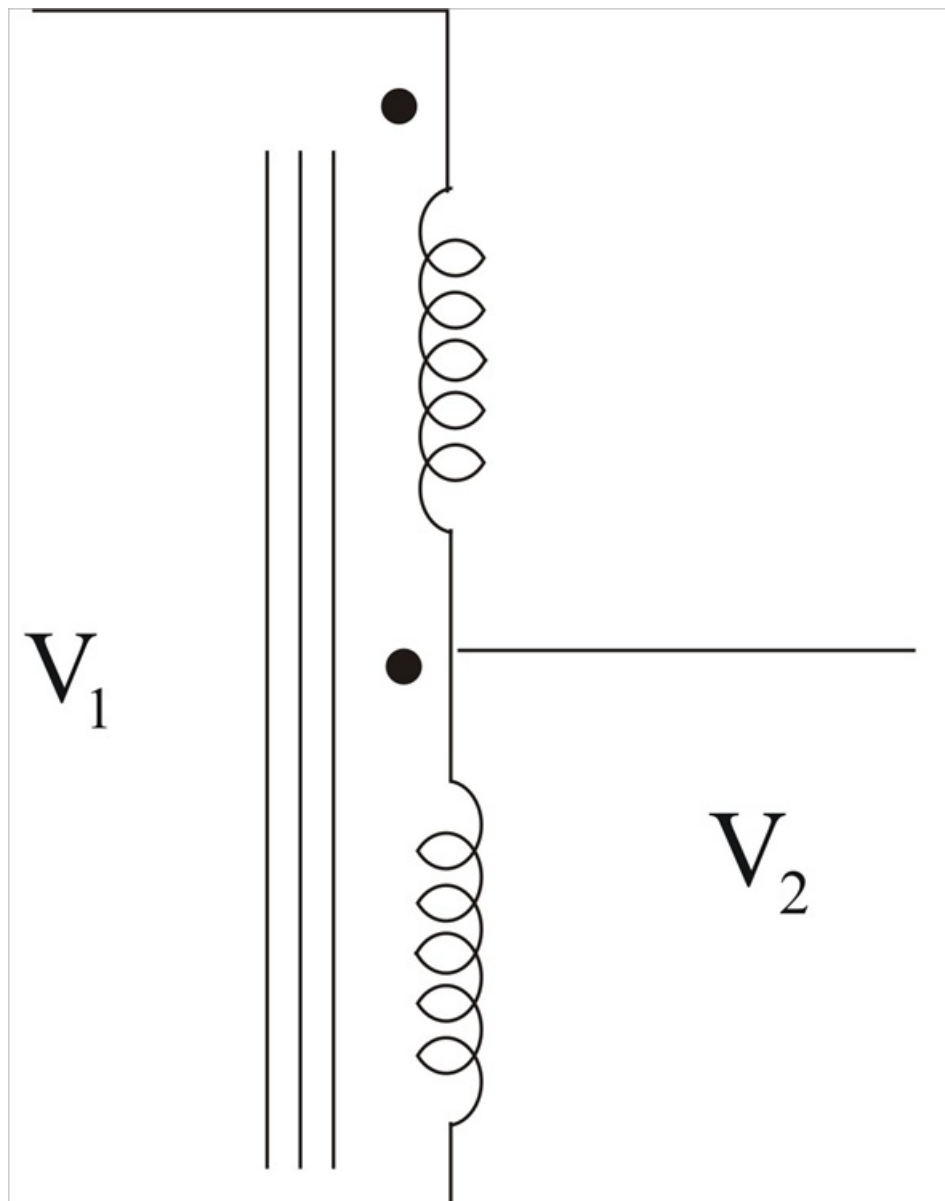

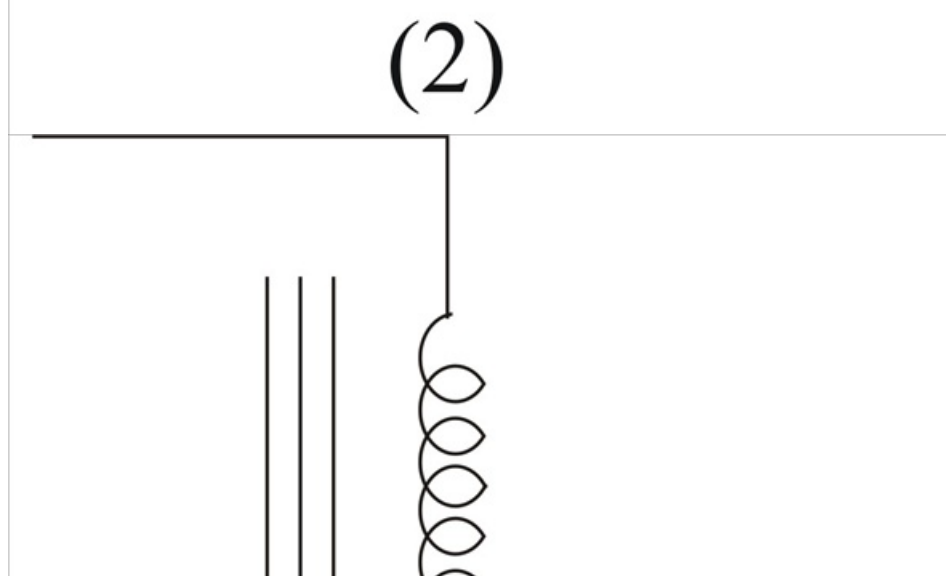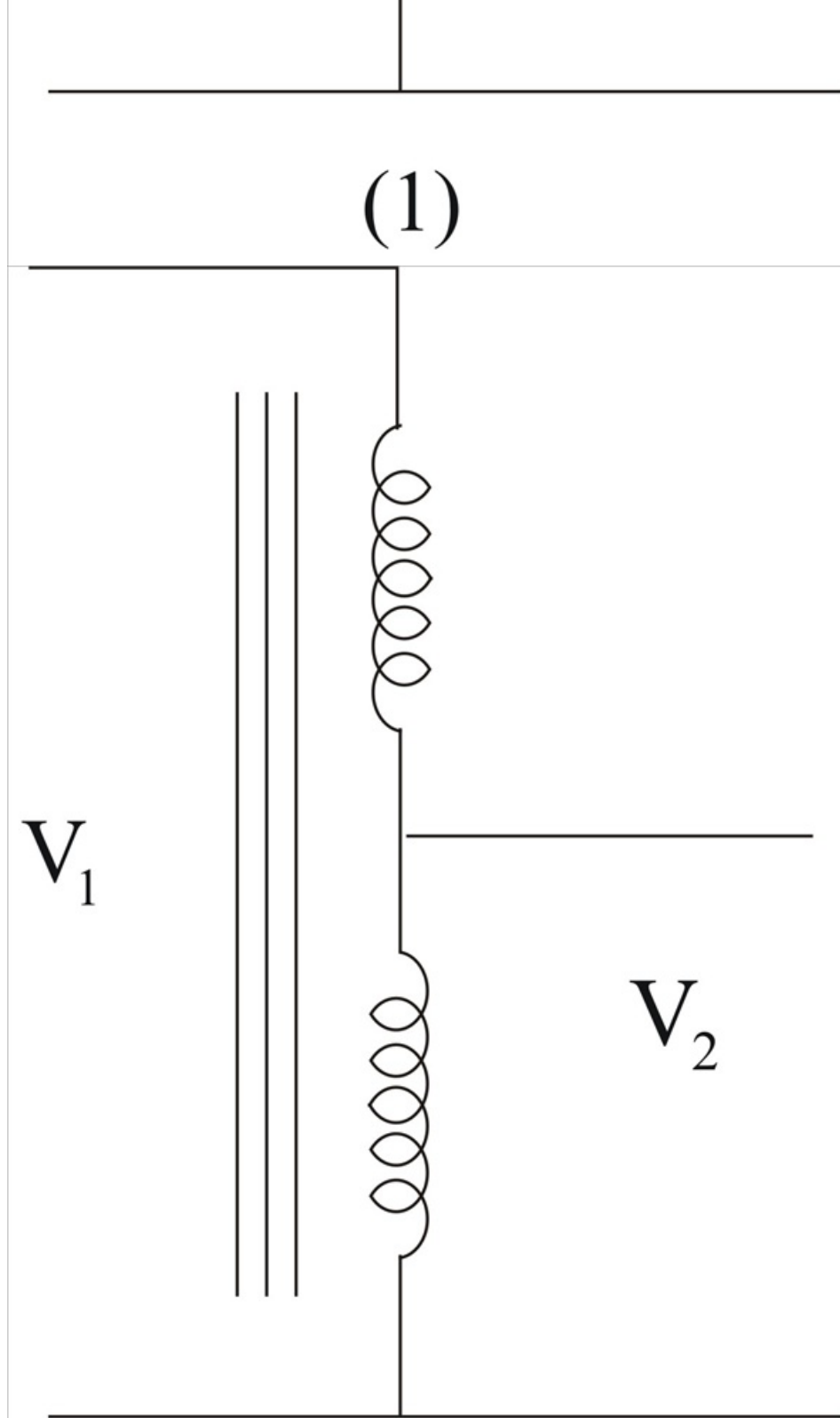

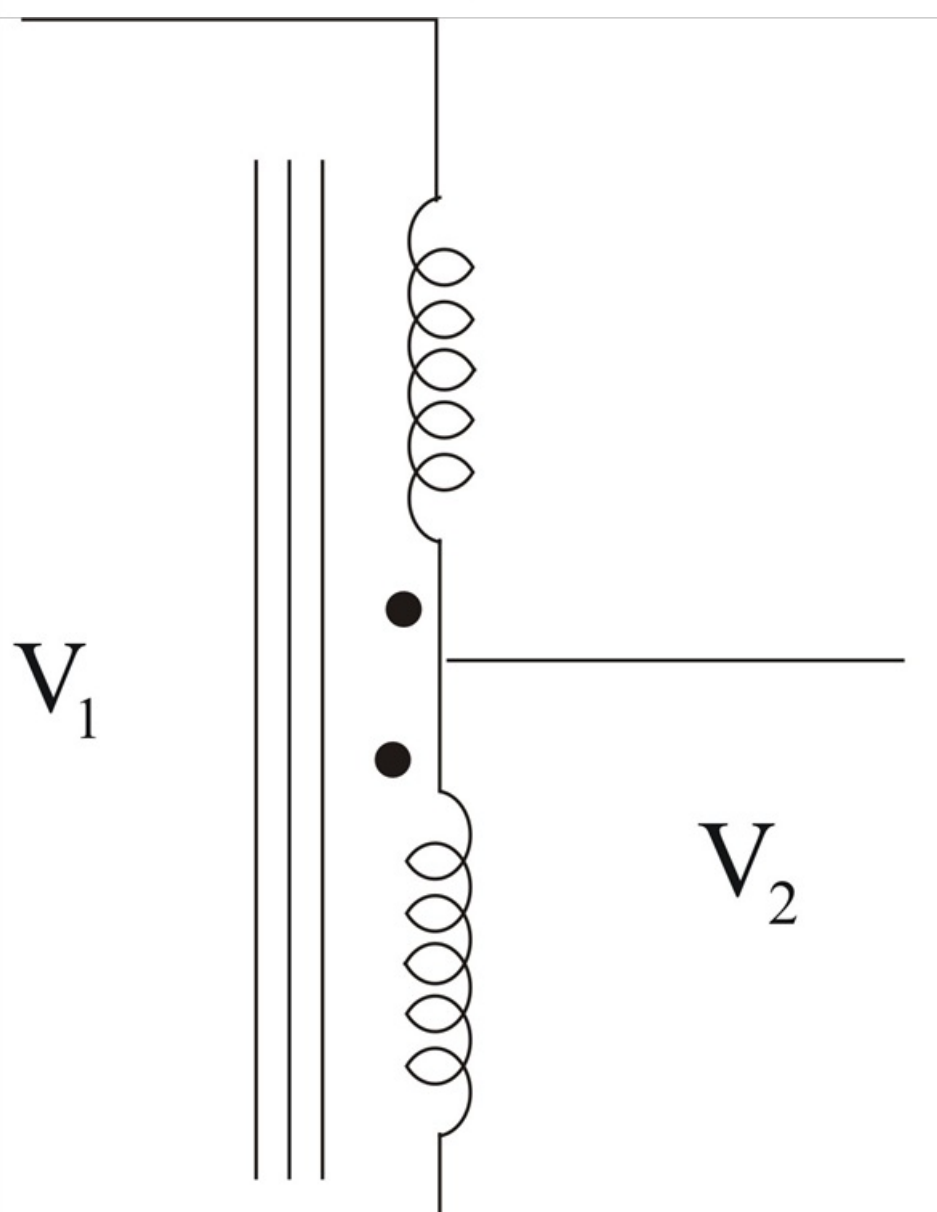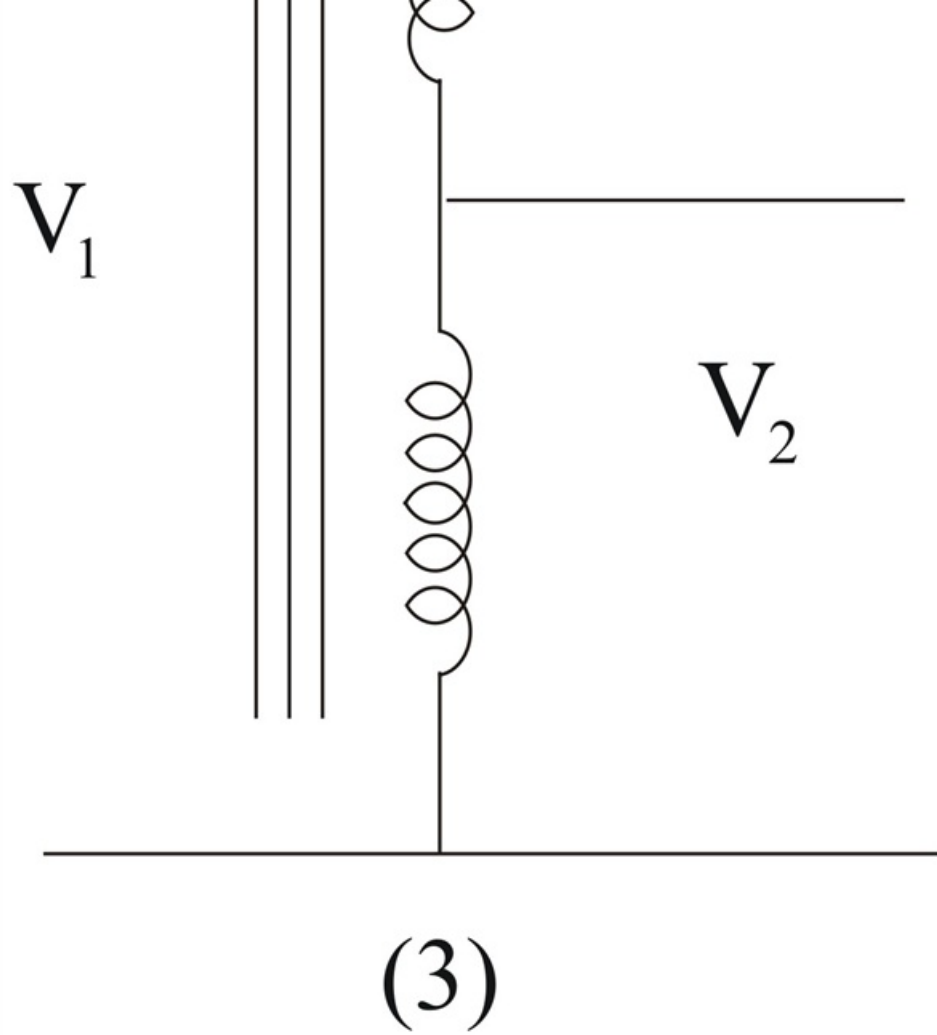

(4)

Step 3 of 5

(1) and (2) produce the same results and (3) and (4) also produce the same results. Therefore, we will only consider figure (1) and (3).

Step 4 of 5

(A) For figure (3),

$$\begin{aligned}\frac{V_1}{V_2} &= \frac{550}{V_2} \\ &= \frac{(440-110)}{440} = \frac{330}{440}\end{aligned}$$

Thus,

$$\begin{aligned}V_2 &= 550 \times \frac{440}{330} \\ &= 733.4 \text{ V}_x \text{ [Not desired result] .}\end{aligned}$$

Step 5 of 5

(B) For figure (1),

$$\begin{aligned}\frac{V_1}{V_2} &= \frac{550}{V_2} \\ &= \frac{(440+110)}{440} = \frac{550}{440}\end{aligned}$$

Thus,

$$\begin{aligned}V_2 &= 550 \times \frac{440}{550} \\ &= 440 \text{ V [The desired result] .}\end{aligned}$$