


Problem

Ten bulbs in parallel are supplied by a 7,200/120-V transformer as shown in Fig. 13.147, where the bulbs are modeled by the $144\text{-}\Omega$ resistors. Find:

(a) the turns ratio n ,

(b) the current through the primary winding.

Figure 13.147

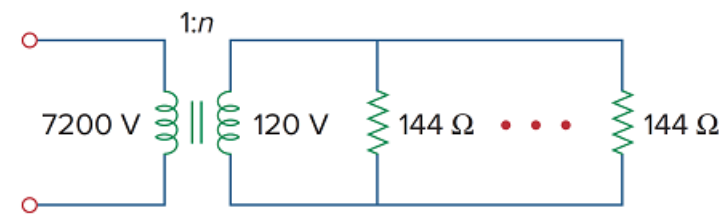

Step-by-step solution

Step 1 of 2

$$\begin{aligned} \text{(A)} \quad n &= \frac{V_s}{V_p} \\ &= \frac{120}{7200} = \frac{1}{60} . \end{aligned}$$

Step 2 of 2

$$\begin{aligned} \text{(B)} \quad I_s &= 10 \times \frac{120}{144} = \frac{1200}{144} \\ S &= V_p I_p = V_s I_s \\ I_p &= \frac{V_s I_s}{V_p} \\ &= \left(\frac{1}{60} \right) \times \frac{1200}{144} \\ I_p &= 139 \text{ mA} . \end{aligned}$$