

Problem

The difference between the half-power frequencies is called the:

- (a) quality factor
- (b) resonant frequency
- (c) bandwidth
- (d) cutoff frequency

Step-by-step solution

Step 1 of 1

The bandwidth is the frequency band between half-power frequencies. It can be expressed mathematically as

$$B = \omega_2 - \omega_1$$

Here,

B is the bandwidth

ω_2, ω_1 are half-power frequencies.

Therefore the difference between the half power frequencies is called bandwidth.

Thus the correct option is (c).

So options $(a), (b)$ and (d) are wrong.