

Problem

In a series RLC circuit, which of these quality factors has the steepest magnitude response curve near resonance?


- (a) $Q = 20$
- (b) $Q = 12$
- (c) $Q = 8$
- (d) $Q = 4$

Step-by-step solution

Step 1 of 4

The series resonant circuit is,

Step 2 of 4

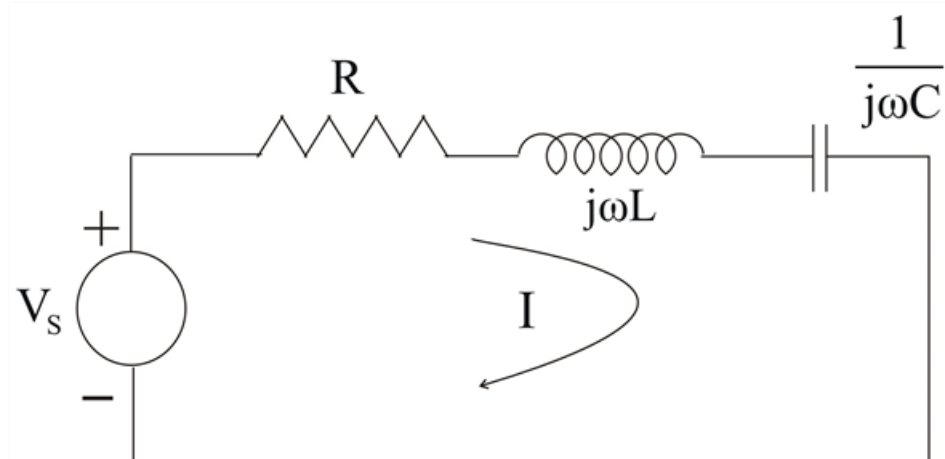

Step 3 of 4

The input impedance is

$$Z = H(\omega) = \frac{V_s}{I} = R + j\omega L + \frac{1}{j\omega C} \quad -(1)$$

$$\text{Or } Z = R + j\left(\omega L - \frac{1}{\omega C}\right) \quad -(2)$$

At resonance, $\omega = \omega_o$

$$I_m = (Z) = 0.$$

$$\omega = \omega_o, \quad \omega L - \frac{1}{\omega C} = 0$$

$$\Rightarrow \omega_o = \frac{1}{\sqrt{LC}} \quad -(3)$$

A Resonant circuit is said to be high quality if quality factor W equal to or greater than 10, ($\theta \geq 10$).

There fore $\theta = 20$ has the steepest curve at resonance

