

Problem

A parallel resonant circuit has $R = 100\text{ k}\Omega$, $L = 50\text{ mH}$, and $C = 2\text{ nF}$. Calculate ω_0 , ω_1 , ω_2 , Q , and B .

Step-by-step solution

Step 1 of 4

Write the expression for the resonance frequency for a parallel RLC circuit.

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Substitute 50 mH for L and 2 nF for C .

$$\begin{aligned}\omega_0 &= \frac{1}{\sqrt{(50 \times 10^{-3})(2 \times 10^{-9})}} \\ &= \frac{1}{\sqrt{100 \times 10^{-12}}} \\ &= \frac{1}{10^{-5}} \\ &= 100\text{ krad/s}\end{aligned}$$

Therefore, the resonant frequency, ω_0 is $\boxed{100\text{ krad/s}}$.

Step 2 of 4

Write the expression for the Quality factor of a parallel RLC circuit.

$$Q = \frac{R}{\omega_0 L}$$

Substitute $100\text{ k}\Omega$ for R , 100 krad/s for ω_0 and 50 mH for L .

$$\begin{aligned}Q &= \frac{100 \times 10^3}{(100 \times 10^3)(50 \times 10^{-3})} \\ &= \frac{1}{50 \times 10^{-3}} \\ &= 20\end{aligned}$$

Therefore, the quality factor, Q of the circuit is $\boxed{20}$.

Step 3 of 4

Calculate the Bandwidth of the circuit.

$$B = \frac{\omega_0}{Q}$$

Substitute 100 krad/s for ω_0 and 20 for Q .

$$\begin{aligned} B &= \frac{100 \times 10^3}{20} \\ &= 5000 \text{ rad/s} \\ &= 5 \text{ krad/s} \end{aligned}$$

Therefore, the bandwidth, B of the circuit is 5 krad/s.

Step 4 of 4

Calculate the half power frequency ω_1 .

$$\omega_1 = \omega_0 - \frac{B}{2}$$

Substitute 100 krad/s for ω_0 and 5 krad/s for B .

$$\begin{aligned} \omega_1 &= 100 \times 10^3 - \frac{5000}{2} \\ &= 100 \times 10^3 - 2500 \\ &= 97.5 \text{ krad/s} \end{aligned}$$

Calculate the half power frequency ω_2 .

$$\omega_2 = \omega_0 + \frac{B}{2}$$

Substitute 100 krad/s for ω_0 and 5 krad/s for B .

$$\begin{aligned} \omega_2 &= 100 \times 10^3 + \frac{5000}{2} \\ &= 100 \times 10^3 + 2500 \\ &= 102.5 \text{ krad/s} \end{aligned}$$

Therefore, the half power frequencies, ω_1 and ω_2 are 97.5 krad/s and 102.5 krad/s.