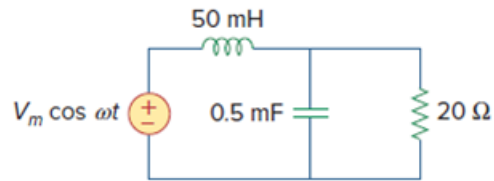


Problem

Calculate the resonant frequency of the circuit in Fig. 14.29.

Figure 14.29:



Step-by-step solution

Step 1 of 3

Refer to circuit diagram in Figure 14.29 in the text book.

The inductor in frequency domain is,

$$\begin{aligned} X_L &= j\omega L \\ &= j\omega(50 \times 10^{-3}) \\ &= 0.05j\omega \end{aligned}$$

The capacitor in frequency domain is,

$$\begin{aligned} X_C &= \frac{1}{j\omega C} \\ &= \frac{1}{j\omega(0.5 \times 10^{-3})} \\ &= \frac{2000}{j\omega} \end{aligned}$$

Step 2 of 3

In the circuit, resistor and capacitor are connected in parallel and this parallel combination is in series with inductor.

Calculate the total admittance of the circuit.

$$\begin{aligned}
 Y &= \left(\frac{1}{X_C} + \frac{1}{R} \right) \left(\frac{1}{X_L} \right) \\
 &= \frac{\frac{1}{X_C} + \frac{1}{R} + \frac{1}{X_L}}{\frac{1}{X_C} + \frac{1}{R} + \frac{1}{X_L}} \\
 &= \frac{\left(\frac{j\omega}{2000} + \frac{1}{20} \right) \left(\frac{1}{0.05j\omega} \right)}{\frac{j\omega}{2000} + \frac{1}{20} + \frac{1}{0.05j\omega}} \\
 &= \frac{\left(\frac{j20\omega + 2000}{40000} \right) \left(\frac{1}{0.05j\omega} \right)}{\frac{-\omega^2 + j100\omega + 40000}{j2000\omega}} \\
 &= \frac{j20\omega + 2000}{-\omega^2 + j100\omega + 40000} \\
 &= \frac{(j20\omega + 2000)(40000 - \omega^2 - j100\omega)}{(40000 - \omega^2 + j100\omega)(40000 - \omega^2 - j100\omega)} \\
 &= \frac{j800000\omega - j20\omega^3 + 2000\omega^2 + 80 \times 10^6 - 2000\omega^2 - j200000\omega}{(40000 - \omega^2 + j100\omega)(40000 - \omega^2 - j100\omega)} \\
 &= \frac{80 \times 10^6 - j(20\omega^3 - 600000\omega)}{(40000 - \omega^2 + j100\omega)(40000 - \omega^2 - j100\omega)}
 \end{aligned}$$

Step 3 of 3

At resonance imaginary part of the admittance is zero.

$$\text{Im}(Y) = 0$$

$$\frac{20\omega^3 - 600000\omega}{(40000 - \omega^2 + j100\omega)(40000 - \omega^2 - j100\omega)} = 0$$

$$20\omega^3 - 600000\omega = 0$$

$$20\omega^3 = 600000\omega$$

$$\omega^2 = 30000$$

$$\omega = 173.21 \text{ rad/s}$$

Therefore, the resonant frequency, ω_0 of the circuit is 173.21 rad/s.