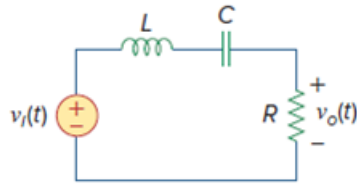


Problem

Design a band-pass filter of the form in Fig. 14.35 with a lower cutoff frequency of 20.1 kHz and an upper cutoff frequency of 20.3 kHz. Take $R = 30 \text{ k}\Omega$. Calculate L , C , and Q .

Figure 14.35: A band-pass filter.



Step-by-step solution

Step 1 of 5

Refer to circuit diagram in Figure 14.35 in the text book.

The lower cutoff frequency is $f_1 = 20.1 \text{ kHz}$, and upper cutoff frequency is $f_2 = 20.3 \text{ kHz}$.

Calculate the Band width in rad/s.

$$\begin{aligned} B &= \omega_2 - \omega_1 \\ &= 2\pi f_2 - 2\pi f_1 \end{aligned}$$

Substitute 20.3 kHz for f_2 and 20.1 kHz for f_1 .

$$\begin{aligned} B &= 2\pi(20.3 \times 10^3) - 2\pi(20.1 \times 10^3) \\ &= 2\pi(0.2 \times 10^3) \\ &= 1256.64 \text{ rad/s} \end{aligned}$$

Step 2 of 5

Write the expression for band width in terms of resistor and inductor.

$$\begin{aligned} B &= \frac{R}{L} \\ L &= \frac{R}{B} \end{aligned}$$

Substitute 1256.64 rad/s for B and $30 \text{ k}\Omega$ for R .

$$\begin{aligned} L &= \frac{30 \times 10^3}{1256.64} \\ &= 23.87 \text{ H} \end{aligned}$$

Therefore, the value of inductor, L is 23.87 H .

Step 3 of 5

Calculate the resonant frequency.

$$\omega_0 = 2\pi\sqrt{f_2 f_1}$$

Substitute 20.3 kHz for f_2 and 20.1 kHz for f_1 .

$$\begin{aligned}\omega_0 &= 2\pi\sqrt{(20.3 \times 10^3)(20.1 \times 10^3)} \\ &= 2\pi\sqrt{408.03 \times 10^6} \\ &= 2\pi(20.19 \times 10^3) \\ &= 126.92 \text{ krad/s}\end{aligned}$$

Step 4 of 5

Write the expression for resonant frequency in terms of inductor and capacitor.

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$LC = \frac{1}{\omega_0^2}$$

$$C = \frac{1}{\omega_0^2 L}$$

Substitute 126.92 krad/s for ω_0 and 23.87 H for L ,

$$\begin{aligned}C &= \frac{1}{(126.92 \times 10^3)^2 (23.87)} \\ &= \frac{1}{384.5 \times 10^9} \\ &= 2.6 \text{ pF}\end{aligned}$$

Therefore, the value of capacitor, C is 2.6 pF.

Step 5 of 5

Write the expression for quality factor.

$$Q = \frac{1}{\omega_0 RC}$$

Substitute 126.92 krad/s for ω_0 , 30 k Ω for R and 2.6 pF for C .

$$\begin{aligned}Q &= \frac{1}{(126.92 \times 10^3)(30 \times 10^3)(2.6 \times 10^{-12})} \\ &= \frac{1}{9.899 \times 10^{-3}} \\ &= 101\end{aligned}$$

Therefore, the value of quality factor is 101.