

Problem

Design a high-pass filter with a high-frequency gain of 5 and a corner frequency of 2 kHz. Use a 50-nF capacitor in your design.

Step-by-step solution

Step 1 of 3

The gain of the high pass filter is,

$$\frac{-R_f}{R_i} = 5$$

Capacitor value is,

$$C_i = 50 \text{ nF}$$

Corner frequency is,

$$f_c = 2 \text{ kHz}$$

Calculate the corner frequency in rad/s.

$$\begin{aligned}\omega_c &= 2\pi f_c \\ &= 2\pi(2 \times 10^3) \\ &= 12.566 \text{ krad/s}\end{aligned}$$

Step 2 of 3

For a high pass filter, the expression for high pass filter in terms of capacitor and resistor is,

$$\omega_c = \frac{1}{R_i C_i}$$

Substitute 12.566 krad/s for ω_c , and 50 nF for C_i in the above equation.

$$\begin{aligned}12.566 \times 10^3 &= \frac{1}{R_i (50 \times 10^{-9})} \\ R_i &= \frac{1}{(12.566 \times 10^3)(50 \times 10^{-9})} \\ &= \frac{1}{628.32 \times 10^{-6}} \\ &= 1591.6 \, \Omega \\ &\cong 1600 \, \Omega\end{aligned}$$

Therefore, the value of resistor, R_i is 1600 Ω .

Step 3 of 3

The gain of the filter is,

$$\frac{R_f}{R_i} = 5$$

Substitute $1600\ \Omega$ for R_i in the above equation.

$$\frac{R_f}{1600\ \Omega} = 5$$

$$\begin{aligned} R_f &= (5)(1600\ \Omega) \\ &= 8\ \text{k}\Omega \end{aligned}$$

Therefore, the value of the resistor R_f is $8\ \text{k}\Omega$.