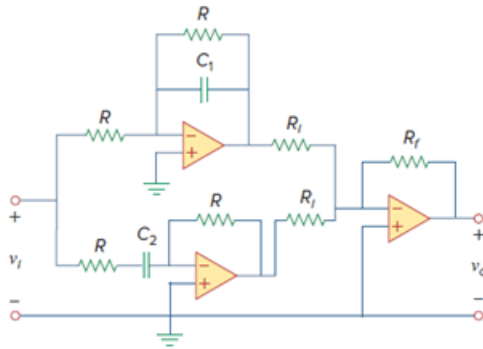


Problem

Design a notch filter based on Fig. 14.47 for $\omega_0 = 20 \text{ krad/s}$, $K = 5$, and $Q = 10$. Use $R = R_i = 10 \text{ k}\Omega$.

Figure 14.47: Active band-reject filter.



Step-by-step solution

Step 1 of 7

Given that,

$$\omega_0 = 20 \text{ k rad / sec}$$


$$K = 5$$

$$Q = 10$$

$$R = R_i = 10 \text{ k}\Omega$$

Step 2 of 7

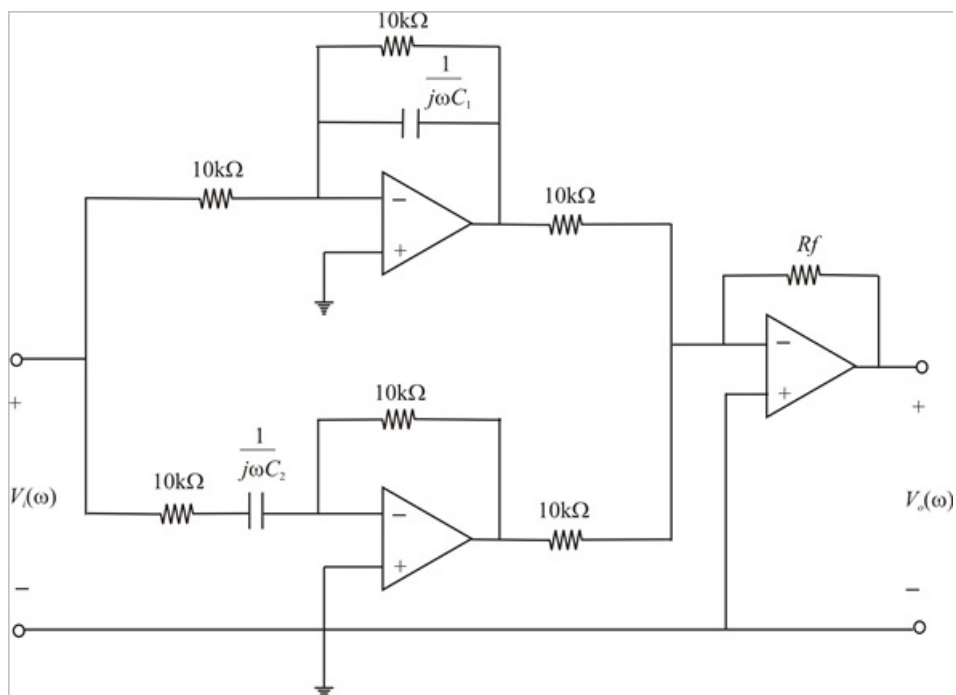A notch filter is designed based on given values as,



Step 3 of 7

We know that,

$$\text{Gain } (K) = \frac{R_f}{R_i}$$

$$\Rightarrow 5 = \frac{R_f}{10 \text{ k}\Omega}$$

$$\therefore \boxed{R_f = 50 \text{ k}\Omega}$$

Step 4 of 7

Quality factor,

$$\Rightarrow Q = \frac{\omega_0}{B}$$

$$\Rightarrow B = \frac{\omega_0}{Q}$$

$$\Rightarrow B = \frac{20 \times 10^3}{10}$$

$$\Rightarrow B = 2000 \text{ rad /sec}$$

Step 5 of 7

$$\text{Band width } (B) = \omega_2 - \omega_1$$

$$2000 = \omega_2 - \omega_1 \dots\dots\dots (1)$$

$$\text{Resonant frequency } (\omega_0) = \sqrt{\omega_1 \omega_2}$$

$$\omega_0^2 = \omega_1 \omega_2$$

$$\Rightarrow (20 \times 10^3)^2 = \omega_1 \omega_2$$

$$\therefore \omega_1 = \frac{400 \times 10^6}{\omega_2} \dots\dots\dots (2)$$

Substitute value of ω_1 in equation (1), then

$$2000 = \omega_2 - \frac{(400 \times 10^6)}{\omega_2}$$

$$2000\omega_2 = \omega_2^2 - (400 \times 10^6)$$

$$\omega_2^2 - 2000\omega_2 - (400 \times 10^6) = 0$$

By using quadratic roots expression, we get

$$\omega_2 = 21.025 \text{ k rad/ sec } \quad (\text{or})$$

$$\omega_2 = -19.025 \text{ k rad/ sec}$$

Step 6 of 7

If we take positive ω_2 and substitute in equation (2), we obtain

$$\omega_2 = \frac{1}{RC_1}$$

$$\Rightarrow C_1 = \frac{1}{\omega_2 R}$$

$$\Rightarrow C_1 = \frac{1}{(21.025 \times 10^3) \times (10 \times 10^3)}$$

$$\therefore \boxed{C_1 = 4.76 \text{ nF}}$$

Step 7 of 7

While the high pas section, the lower corner frequency is,

$$\omega_1 = \frac{1}{RC_2}$$

$$\Rightarrow C_2 = \frac{1}{\omega_1 R}$$

$$\Rightarrow C_2 = \frac{1}{(19.025 \times 10^3) (10 \times 10^3)}$$

$$\therefore \boxed{C_2 = 5.26 \text{ nF}}$$