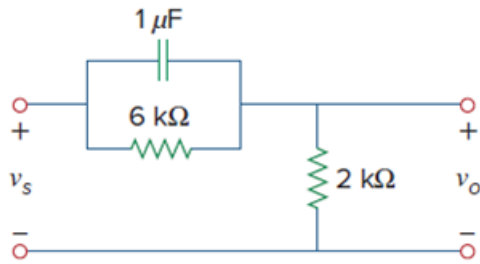


Problem

Obtain the frequency response of the circuit in Fig. 14.53 using *PSpice*. Use a linear frequency sweep and consider $1 < f < 1,000$ Hz with 100 points.

Figure 14.53:




Step-by-step solution

Step 1 of 7

Step (1)

We use schematic to create the circuit and double click on each component and enter the given values, as shown in below circuit here we use VAC voltage source from the source library and double click on VAC voltage source and set DC = 0V and AC MAG = 1V and AC PHASE = 0°

Step 2 of 7

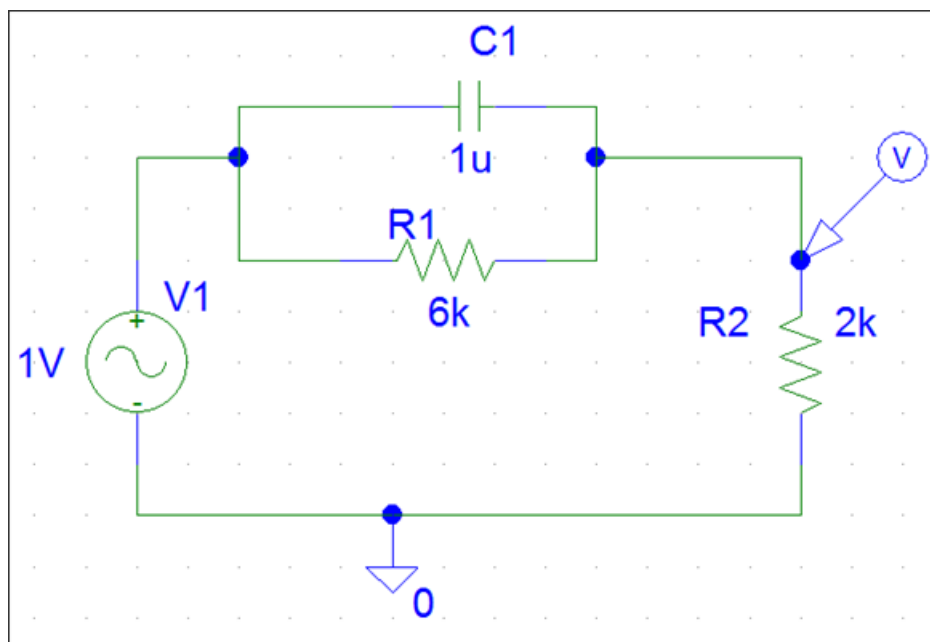

Step 3 of 7

Step (2)

In the simulation analysis, select AC sweep and enter the starting frequency = 1Hz, end frequency = 1000 and total points / decade = 100.


Step 4 of 7

Step (3)

Got 'analysis' menu open 'simulate' (or press 'F – 11')

The result magnitude plot is

Step 5 of 7

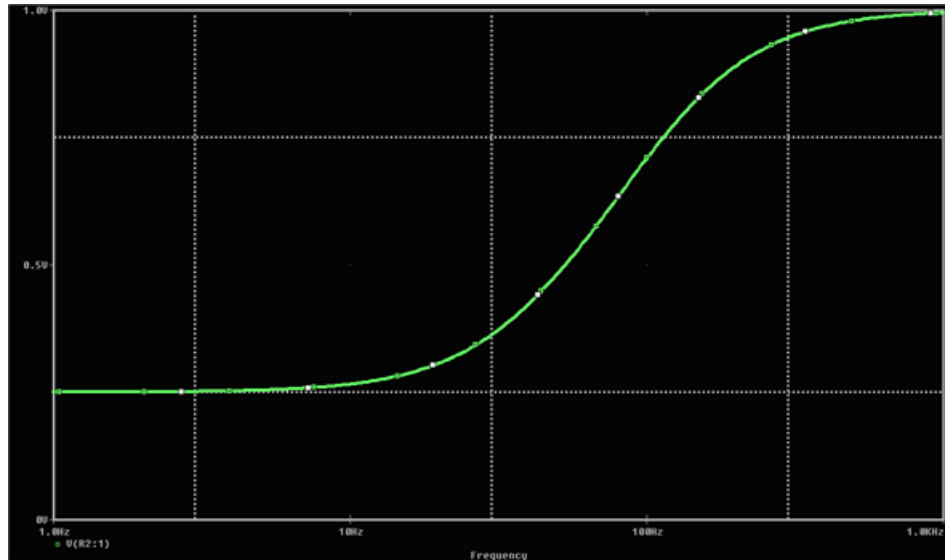

Step 6 of 7

Step (4)

To obtain the phase plot, select trace / add in PSpice A/D Demo menu and type $VP(R2:1)$ in the trace command box.

Step 7 of 7

