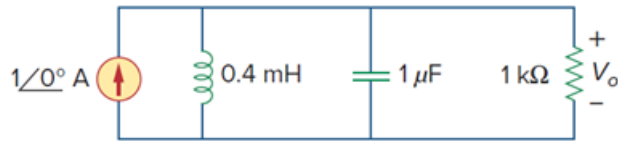


## Problem

Consider the network in Fig. 14.57. Use *PSpice* to obtain the Bode plots for  $V_o$  over a frequency from 1 to 100 kHz using 20 points per decade.

**Figure 14.57:**



## Step-by-step solution


## Step 1 of 7

Step 1:

We use schematics to create the circuit, and double click on each component and enter the given values as shown in below circuit.

Here, we use VAC voltage source from the source library and double click on VAC voltage source and set DC = 0V, AC MAG = 1V and ACPHASE = 00

## Step 2 of 7

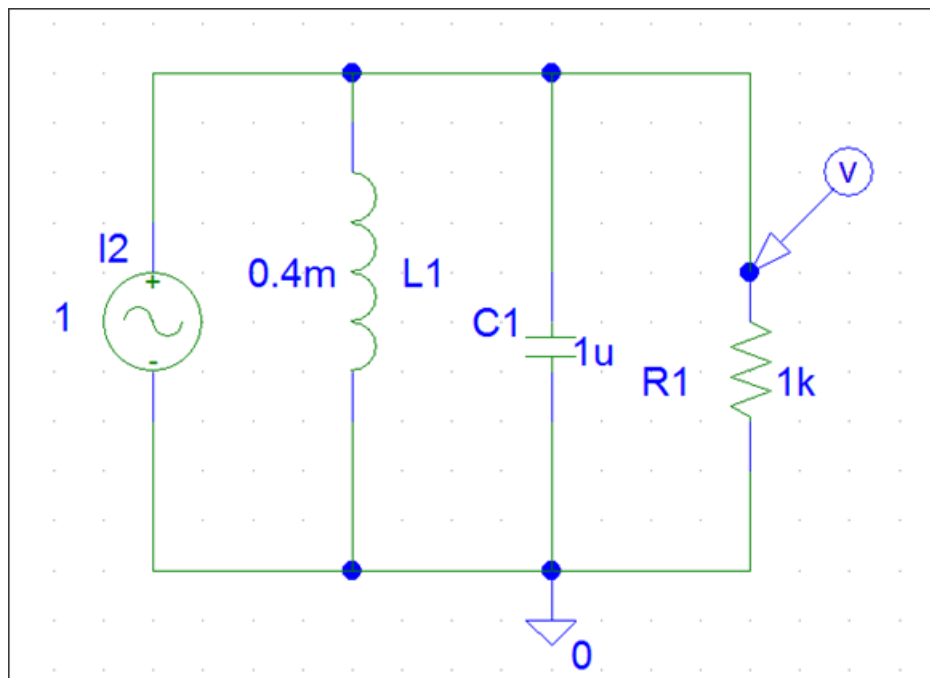

## Step 3 of 7

Step 2:

In the simulation analysis, select AC sweep, and enter the starting frequency = 1 kHz and frequency = 100 kHz and total points/decade = 20


#### Step 4 of 7

Step 3:

Go to 'Analysis' menu open 'simulate' (or press 'F- 11')

The resultant magnitude plot is

#### Step 5 of 7

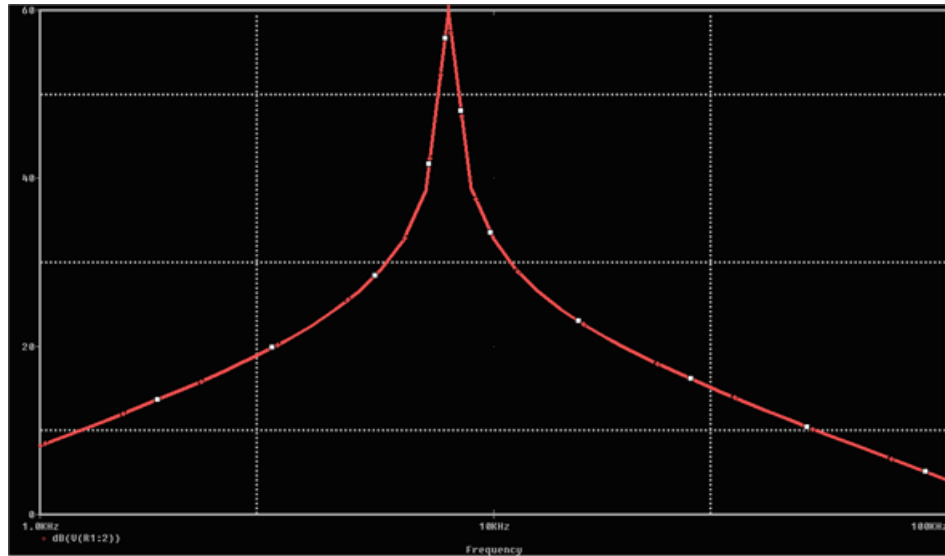

#### Step 6 of 7

Step 4:

To obtain the phase plot we select **trace / add** in PSpice A/D demo menu and type VP(R1:2) in the trace command box. The resultant bode phase plot is

#### Step 7 of 7

