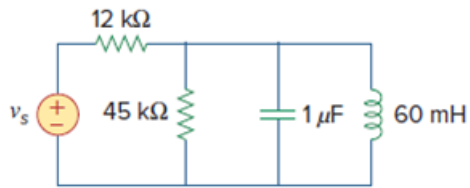


Problem

Let $v_s = 20 \cos(at)$ V in the circuit of Fig. 14.77. Find ω_0 , Q , and B , as seen by the capacitor.


Figure 14.77:



Step-by-step solution

Step 1 of 7

Consider the following circuit diagram:

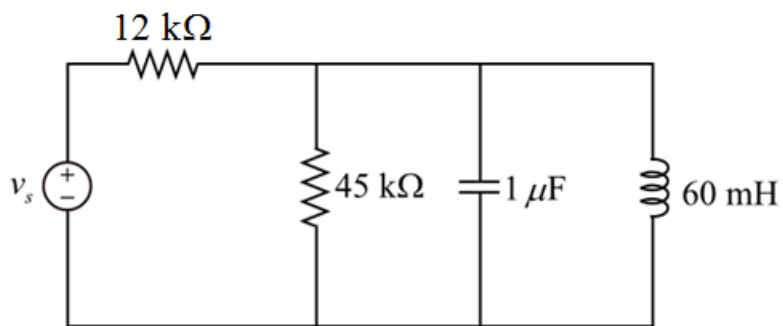

Step 2 of 7

Figure 1

Step 3 of 7

Consider the following data:

Input voltage $v_s = 20 \cos(at)$ V.

Step 4 of 7

A source transformation is the process of replacing a voltage source v_s in series with a resistor R by a current source i_s in parallel with a resistor R , or vice versa.

Apply source transformation to the circuit, we will get current source i_s in parallel with a resistor $12\text{ k}\Omega$ as shown below.

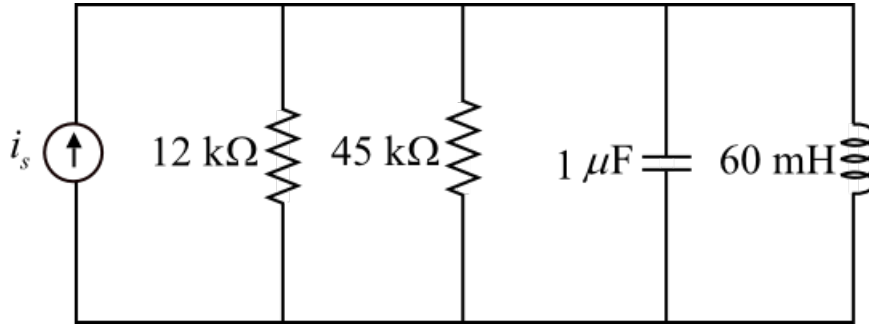



Figure 2

Step 5 of 7

To get equivalent resistance R , we combine resistors in parallel and in series. The $45\text{ k}\Omega$ and $12\text{ k}\Omega$ resistors are in parallel. So their equivalent resistance is:

$$\begin{aligned} R &= 45\text{ k}\Omega \parallel 12\text{ k}\Omega \\ &= \frac{45\text{ k} \times 12\text{ k}}{45\text{ k} + 12\text{ k}} \\ &= 9.47\text{ k}\Omega \end{aligned}$$

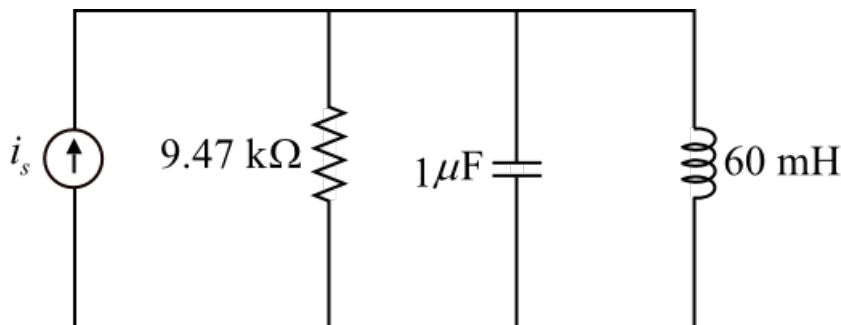Redraw, figure 2 by replacing resistors $45\text{ k}\Omega$ and $12\text{ k}\Omega$ with equivalent resistance $9.47\text{ k}\Omega$.



Step 6 of 7

Figure 3 is a parallel RLC circuit. Thus

Write the expression for resonant frequency ω_0 .

$$\begin{aligned} \omega_0 &= \frac{1}{\sqrt{LC}} \\ &= \frac{1}{\sqrt{(60 \times 10^{-3})(1 \times 10^{-6})}} \\ &= \frac{1}{\sqrt{6 \times 10^{-8}}} \\ &= \frac{1}{0.244 \times 10^{-3}} \\ &= 4082.48\text{ rad/s} \\ &= 4.082\text{ krad/s} \end{aligned}$$

Thus, resonant frequency ω_0 is 4.082 krad/s.

Write the expression for quality factor of a parallel resonance circuit:

$$Q = \omega_0 RC$$

Substitute $9.47 \text{ k}\Omega$ for R , 1μ for C and 4082.48 for ω_0 in the expression $\omega_0 RC$ to get the quality factor.

$$Q = (4082.4)(9.47 \times 10^3)(1 \times 10^{-6})$$

$$\cong 38.67$$

Therefore the quality factor Q is $\boxed{38.67}$.

Write the expression for bandwidth of the circuit.

$$B = \frac{\omega_0}{Q}$$

Substitute 38.67 for Q and 4082.48 for ω_0 values in the above expression.

$$B = \frac{4082}{38.67}$$

$$= 105.55 \text{ rad/s}$$

Therefore the bandwidth of the circuit is $\boxed{105.55 \text{ rad/s}}$.