

Problem

A parallel RLC circuit has $R = 10\text{ k}\Omega$, $L = 100\text{ mH}$, and a resonant frequency of 200 krad/s . Calculate the value of C , the value of the quality factor, and the bandwidth.

Step-by-step solution

Step 1 of 3

Write the formula for resonant frequency.

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Substitute 100 mH for L and 200 krad/s for ω_0 .

$$200 \times 10^3 = \frac{1}{\sqrt{100 \times 10^{-3} \times C}}$$

$$200 \times 10^3 = \frac{1}{\sqrt{0.1C}}$$

$$4 \times 10^{10} = \frac{1}{0.1C}$$

$$\begin{aligned} C &= \frac{1}{0.1(4 \times 10^{10})} \\ &= 250 \times 10^{-12}\text{ F} \\ &= 250\text{ pF} \end{aligned}$$

Therefore, the value of the capacitance, C is $\boxed{250\text{ pF}}$.

Step 2 of 3

Calculate the quality factor of a parallel RLC circuit.

$$Q = \omega_0 RC$$

Substitute 200 krad/s for ω_0 , $10\text{ k}\Omega$ for R and 250 pF for C .

$$\begin{aligned} Q &= \omega_0 RC \\ &= (200 \times 10^3)(10 \times 10^3)(250 \times 10^{-12}) \\ &= 0.5 \end{aligned}$$

Therefore, the quality factor, Q of the circuit is $\boxed{0.5}$.

Calculation of quality factor using alternate formula:

$$Q = \frac{R}{\omega_0 L}$$

Substitute 200 krad/s for ω_0 , $10\text{ k}\Omega$ for R and 100 mH for L .

$$\begin{aligned} Q &= \frac{10 \times 10^3}{(200 \times 10^3)(100 \times 10^{-3})} \\ &= 0.5 \end{aligned}$$

Therefore, the quality factor, Q of the circuit is $\boxed{0.5}$.

Step 3 of 3

Calculate the bandwidth.

$$\begin{aligned} B &= \frac{\omega_0}{Q} \\ &= \frac{200 \times 10^3}{0.5} \\ &= 400 \text{ krad/s} \end{aligned}$$

Therefore, the bandwidth, B of the circuit is 400 krad/s.