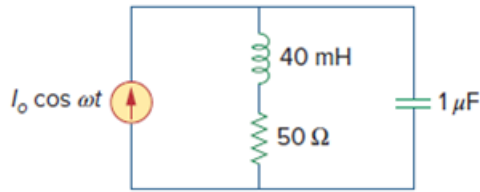


Problem

For the “tank” circuit in Fig. 14.79, find the resonant frequency.

Figure 14.79:



Step-by-step solution

Step 1 of 3

Refer to Figure 14.79 in the textbook.

The impedance of inductor is $j\omega L$.

The impedance of capacitor is $\frac{1}{j\omega C}$.

Redraw the circuit with their impedance values as shown in Figure 1.

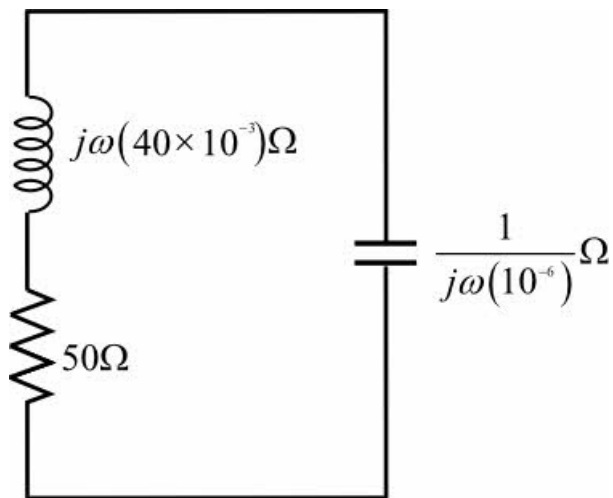


Figure 1

Step 2 of 3

Calculate the input admittance.

$$\begin{aligned}
 Y &= \frac{1}{50 + j\omega(40 \times 10^{-3})} + \frac{1}{\frac{1}{j\omega(10^{-6})}} \\
 &= \frac{1}{50 + j\omega(40 \times 10^{-3})} + j\omega(10^{-6}) \\
 &= \frac{50 - j\omega(40 \times 10^{-3})}{(50)^2 + (40 \times 10^{-3})^2} + j\omega(10^{-6})
 \end{aligned}$$

Simplify further.

$$\begin{aligned} Y &= \frac{50}{(50)^2 + (40\omega \times 10^{-3})^2} - \frac{j\omega(40 \times 10^{-3})}{(50)^2 + (40\omega \times 10^{-3})^2} + j\omega(10^{-6}) \\ &= \frac{50}{(50)^2 + (40\omega \times 10^{-3})^2} + j \left(10^{-6}\omega - \frac{\omega(40 \times 10^{-3})}{(50)^2 + (40\omega \times 10^{-3})^2} \right) \end{aligned}$$

At resonance imaginary part of Y is zero.

$$\text{Im}(Y) = 0$$

$$10^{-6}\omega_0 - \frac{\omega_0(40 \times 10^{-3})}{(50)^2 + (40\omega_0^2 \times 10^{-3})^2} = 0$$

$$10^{-3} - \frac{(40)}{(50)^2 + (40\omega_0^2 \times 10^{-3})^2} = 0$$

$$\left((50)^2 + (40\omega_0^2 \times 10^{-3})^2 \right) 10^{-3} - 40 = 0$$

Simplify further.

$$2.5 + 16 \times 10^{-7} \omega_0^2 = 40$$

$$16 \times 10^{-7} \omega_0^2 = 37.5$$

$$\omega_0 = 4.841 \frac{\text{krad}}{\text{s}}$$

Therefore, the resonant frequency is $\boxed{4.841 \frac{\text{krad}}{\text{s}}}$.