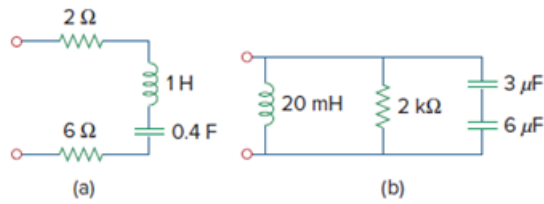


## Problem

For the circuits in Fig. 14.81, find the resonant frequency  $\omega_0$ , the quality factor  $Q$ , and the bandwidth  $B$ .

**Figure 14.81:**



## Step-by-step solution

## Step 1 of 2

(a) This is series RLC circuit

$$R = 2 + 6 = 8\ \Omega$$

$$L = 1\text{ H}$$

$$C = 0.4\text{ F}$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.4}} = 1.5811\text{ rad/s}$$

$$\theta = \frac{\omega_o L}{R} = \frac{1.5811}{8} = 0.1976$$

$$B = \frac{R}{L} = 8\text{ rad/s}$$

## Step 2 of 2

(b) This is a parallel RLC circuit

$$3\ \mu\text{F} \text{ and } 6\ \mu\text{F} \rightarrow \frac{3 \times 6}{3 + 6} = 2\ \mu\text{F}$$

$$C = 2\ \mu\text{F} \quad R = 2\text{ k}\Omega \quad L = 20\text{ mH}$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(2 \times 10^{-6})(20 \times 10^{-3})}} = 5\text{ K rad/s}$$

$$\theta = \frac{R}{\omega_o L} = \frac{2 \times 10^3}{(5 \times 10^3)(20 \times 10^{-3})} = 20$$

$$B = \frac{1}{RC} = \frac{1}{(2 \times 10^3)(2 \times 10^{-6})} = 250\text{ rad/s}$$