

Problem

Show that a series LR circuit is a low-pass filter if the output is taken across the resistor. Calculate the corner frequency f_c if $L = 2 \text{ mH}$ and $R = 10 \text{ k}\Omega$.

Step-by-step solution

Step 1 of 8

Consider the following circuit diagram:

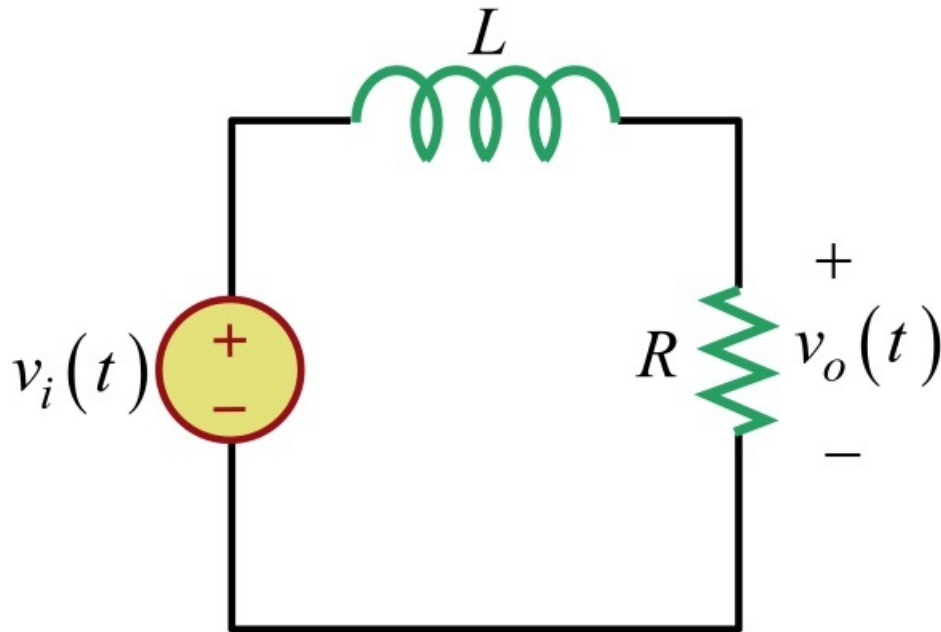


Figure 1

Step 2 of 8

Calculate the transfer function $\mathbf{H}(\omega)$.

Write the expression for the transfer function $\mathbf{H}(\omega)$.

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} \dots\dots (1)$$

Draw the following circuit diagram to find the output voltage $\mathbf{V}_o$.

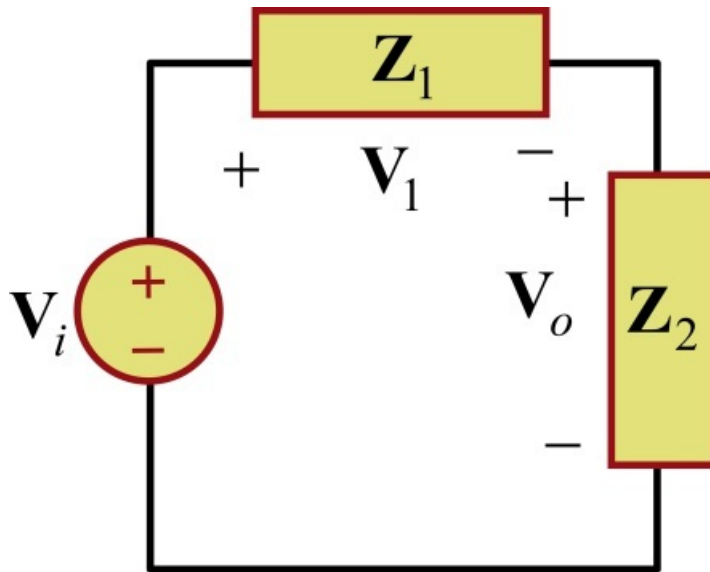


Figure 2

Step 3 of 8

Calculate the output voltage $\mathbf{V}_o$.

Apply voltage division rule across the impedance $\mathbf{Z}_2$ to find the output voltage $\mathbf{V}_o$.

$$\mathbf{V}_o = \frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} \mathbf{V}_i$$

Substitute R for $\mathbf{Z}_2$, $j\omega L$ for $\mathbf{Z}_1$ in this expression.

$$\frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{R}{j\omega L + R}$$

Substitute equation 1 in this expression.

$$\mathbf{H}(\omega) = \frac{1}{1 + j\omega \left(\frac{L}{R} \right)} \dots\dots (1)$$

Therefore, the transfer function $\mathbf{H}(\omega)$ is $\frac{1}{1 + j\omega \left(\frac{L}{R} \right)}$.

Step 4 of 8

Calculate the value of $\mathbf{H}(0)$.

Substitute 0 for ω in the equation 1.

$$\begin{aligned} \mathbf{H}(0) &= \frac{1}{1 + j(0) \left(\frac{L}{R} \right)} \\ &= 1 \end{aligned}$$

Therefore, the value of $\mathbf{H}(0)$ is 1.

Step 5 of 8

Calculate the value of $\mathbf{H}(\infty)$.

Substitute ∞ for ω in the equation 1.

$$\begin{aligned}\mathbf{H}(\infty) &= \frac{1}{1 + j(\infty)\left(\frac{L}{R}\right)} \\ &= \frac{1}{\infty} \\ &= 0\end{aligned}$$

Therefore, the value of $\mathbf{H}(\infty)$ is 0.

Step 6 of 8

The values $\mathbf{H}(0)$ and $\mathbf{H}(\infty)$ are 1, 0 respectively, which corresponds to the ideal characteristics of a Lowpass filter.

Hence, the series LR circuit is a low pass filter when the output is taken across the resistor as shown in Figure 1.

Draw the following circuit diagram:

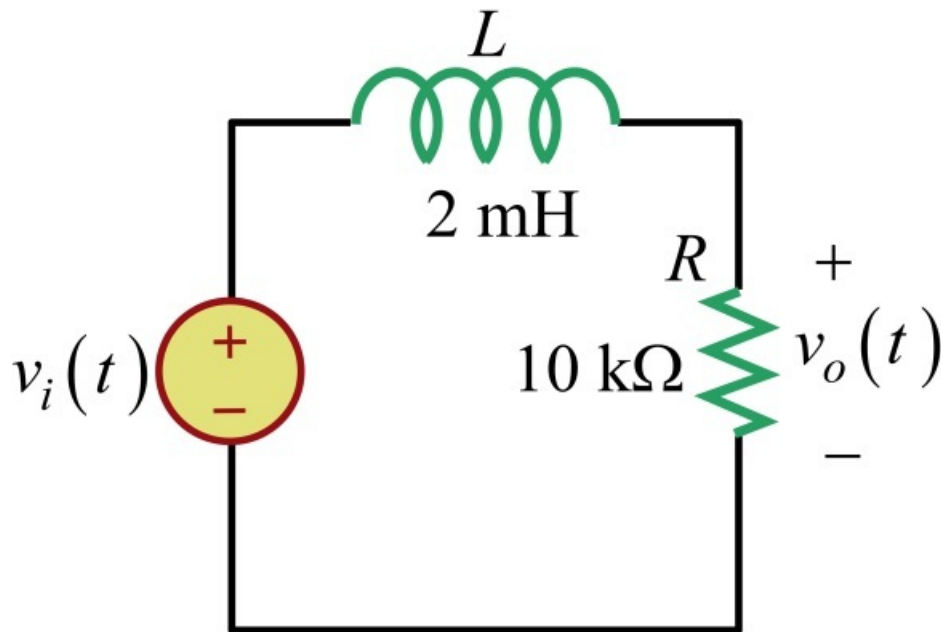


Figure 3

Step 7 of 8

Calculate the magnitude of the transfer function $\mathbf{H}(\omega)$.

Write the expression for the magnitude of the transfer function $\mathbf{H}(\omega)$.

$$\begin{aligned} |\mathbf{H}(\omega)| &= \left| \frac{1}{1 + j\omega \left(\frac{L}{R} \right)} \right| \\ &= \frac{1}{\left| 1 + j\omega \left(\frac{L}{R} \right) \right|} \\ |\mathbf{H}(\omega)| &= \frac{1}{\sqrt{1 + \omega^2 \left(\frac{L}{R} \right)^2}} \dots\dots (2) \end{aligned}$$

Therefore, the magnitude of transfer function $\mathbf{H}(\omega)$ is $\frac{1}{\sqrt{1 + \omega^2 \left(\frac{L}{R} \right)^2}}$.

Step 8 of 8

Calculate the value of the corner frequency f_c of the circuit in Figure 3.

The corner frequency is the frequency at which the magnitude of transfer function $\mathbf{H}(\omega)$ is $\frac{1}{\sqrt{2}}$.

Substitute $\frac{1}{\sqrt{2}}$ for $|\mathbf{H}(\omega)|$ in the equation 2.

$$\begin{aligned} \frac{1}{\sqrt{2}} &= \frac{1}{\sqrt{1 + \omega_c^2 \left(\frac{L}{R} \right)^2}} \\ 1 + \omega_c^2 \left(\frac{L}{R} \right)^2 &= 2 \\ \omega_c^2 \left(\frac{L}{R} \right)^2 &= 1 \\ \omega_c &= \frac{R}{L} \end{aligned}$$

Substitute $2\pi f_c$ for ω_c in this expression.

$$\begin{aligned} (2\pi f_c) &= \frac{R}{L} \\ f_c &= \frac{R}{L(2\pi)} \end{aligned}$$

Substitute 2 mH for L , 10 k Ω for R in this expression.

$$\begin{aligned} f_c &= \frac{10 \times 10^3}{2 \times 10^{-3} (2\pi)} \\ &= 0.7954 \times 10^6 \\ &\cong 796 \times 10^3 \end{aligned}$$

Therefore, the value of corner frequency f_c is **796 kHz**.