

Problem

(a) Show that for a band-pass filter,

$$\mathbf{H}(s) = \frac{sB}{s^2 + sB + \omega_0^2}, \quad s = j\omega$$

where B = bandwidth of the filter and ω_0 is the center frequency.

(b) Similarly, show that for a band-stop filter,

$$\mathbf{H}(s) = \frac{s^2 + \omega_0^2}{s^2 + sB + \omega_0^2}, \quad s = j\omega$$


Step-by-step solution

Step 1 of 6

Consider Band pass filter

Step 2 of 6

(a)

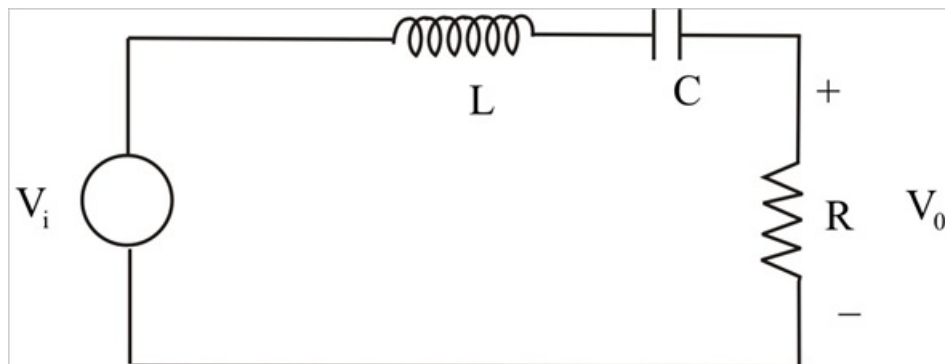

Step 3 of 6

Transfer function is $H(\omega) = \frac{V_o}{V_i} \quad -(1)$

In given circuit, transfer function is

$$H(\omega) = \frac{R}{R + j\left(\omega L - \frac{1}{\omega C}\right)} \quad -(2)$$

$$\text{or, } H(\omega) = \frac{Rj\omega C}{Rj\omega C + j^2\omega^2 L + 1} \quad -(3)$$

Put $j\omega = s$. in (3) we get

$$H(s) = \frac{SRC}{SRC + s^2 L + 1}.$$

Divide by LC

$$H(s) = \frac{S\left(\frac{R}{L}\right)}{S\left(\frac{R}{L}\right) + s^2 + \frac{1}{LC}} \quad -(4)$$

$$\text{we know, } B = \frac{R}{L}, \quad \text{and} \quad \omega_o^2 = \frac{1}{LC} \quad -(5)$$

From (4) and (5) we get

$$\boxed{H(s) = \frac{SB}{s^2 + SB + \omega_o^2}.$$


Step 4 of 6

(b) Consider Band stop filter.

Transfer function is given by $H(\omega)$

$$\begin{aligned} H(\omega) &= \frac{V_o}{V_i} = \frac{\left(j\omega L + \frac{1}{j\omega C}\right)}{R + j\omega L + \frac{1}{j\omega C}} \\ &= \frac{j^2\omega^2 LC + 1}{j\omega CR + j^2\omega^2 LC + 1} \end{aligned}$$

Step 5 of 6

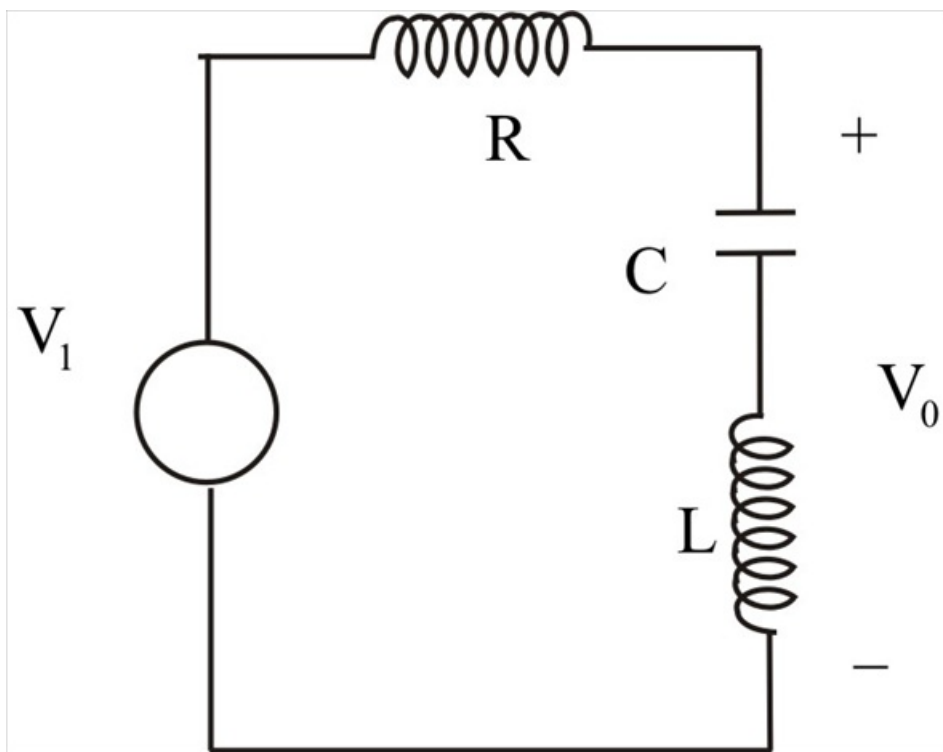

Step 6 of 6

$$= \frac{\mathcal{LC} \left(j^2 \omega^2 + \frac{1}{LC} \right)}{\mathcal{LC} \left(\frac{j\omega L R}{L} + j^2 \omega^2 + \frac{1}{LC} \right)}.$$

$$\boxed{H(\omega) = \frac{S^2 + \omega_o^2}{SB + S^2 + \omega_o^2}} \text{ proved.}$$

$$\text{where, } S = j\omega \quad B = \frac{R}{L} \quad \omega_o^2 = \frac{1}{LC}$$