

Problem

The circuit parameters for a series RLC bandstop filter are $R = 250\ \Omega$, $L = 1\ \text{mH}$, $C = 40\ \text{pF}$. Calculate:

(a) the center frequency

(b) the half-power frequencies

(c) the quality factor

Step-by-step solution

Step 1 of 3

(a)

Calculate the center frequency of band-stop filter.

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Substitute $1\ \text{mH}$ for L and $40\ \text{pF}$ for C .

An RLC band stop filter has the following parameters $R = 250\ \Omega, L = 1\ \text{mH}, C = 40\ \text{pF}$

(a)

Centre frequency is given by

$$\begin{aligned}\omega_0 &= \frac{1}{\sqrt{(10^{-3})(40 \times 10^{-12})}} \\ &= \frac{1}{2 \times 10^{-7}} \\ &= 5\ \text{Mrad/s}\end{aligned}$$

Therefore, the center frequency, ω_0 is 5 Mrad/s.

Step 2 of 3

(b)

Calculate the Bandwidth.

$$\begin{aligned} B &= \frac{R}{L} \\ &= \frac{250}{1 \times 10^{-3}} \\ &= 250 \text{ krad/s} \end{aligned}$$

Calculate the half power frequencies.

$$\begin{aligned} \omega_1 &= \omega_0 - \frac{B}{2} \\ &= 5000 \times 10^3 - \frac{250 \times 10^3}{2} \\ &= 4.875 \text{ Mrad/s} \end{aligned}$$

And,

$$\begin{aligned} \omega_2 &= \omega_0 + \frac{B}{2} \\ &= 5000 \times 10^3 + \frac{250 \times 10^3}{2} \\ &= 5.125 \text{ Mrad/s} \end{aligned}$$

Hence, the half power frequencies are 4.875 Mrad/s, and 5.125 Mrad/s.

Step 3 of 3

(c)

Calculate the quality factor.

$$\begin{aligned} Q &= \frac{\omega_0}{B} \\ &= \frac{5 \times 10^6}{250 \times 10^3} \\ &= 20 \end{aligned}$$

Hence, the quality factor, Q is 20.