

Problem

In an RLC circuit, $R = 20\ \Omega$, $L = 4\ \text{H}$, and $C = 1\ \text{F}$. The circuit is magnitude-scaled by 10 and frequency-scaled by 105. Calculate the new values of the elements.

Step-by-step solution

Step 1 of 1

$$R' = K_m R = 20 \times 10 = 200\ \Omega$$

$$L' = \frac{K_m}{K_f} \omega = \frac{10}{10^5} (4) = 400\ \mu\text{H}$$

$$C' = \frac{C}{K_m K_f} = \frac{1}{10 \times 10^5} = 1\ \mu\text{F}$$