

Problem

A series RLC circuit has $R = 10\ \Omega$, $\omega_0 = 40\text{ rad/s}$, and $B = 5\text{ rad/s}$. Find L and C when the circuit is scaled:

(a) in magnitude by a factor of 600,

(b) in frequency by a factor of 1,000,

(c) in magnitude by a factor of 400 and in frequency by a factor of 105.

Step-by-step solution

Step 1 of 4

L and C are needed before scaling

$$B = \frac{R}{L} \rightarrow L = \frac{R}{B} = \frac{10}{5} = 2H_z$$

$$\omega_o = \frac{1}{\sqrt{LC}} \rightarrow C = \frac{1}{\omega_o^2 L} = \frac{1}{(1000)(2)} = 312.5\mu F$$

[Comments \(1\)](#)



Anonymous

w is given: 40 rad/sec so ω^2 is 1600, not 1000

Step 2 of 4

$$(a) \ L' = K_m L = (600)(2) = 1200H_z$$

$$C' = \frac{C}{K_m} = \frac{3.125 \times 10^{-4}}{600} = 0.5208\mu F$$

Step 3 of 4

$$(b) \ L' = \frac{L}{K_f} = \frac{2}{10^3} = 2mH_z$$

$$C' = \frac{C}{K_f} = \frac{3.125 \times 10^{-4}}{10^3} = 312.5nF$$

Step 4 of 4

$$(c) \ L' = \frac{K_m}{K_f} L = \frac{(400)(2)}{10^5} = 8mH_z$$

$$C' = \frac{C}{K_m K_f} = \frac{3.125 \times 10^{-4}}{(400)(10^5)} = 7.81PF$$