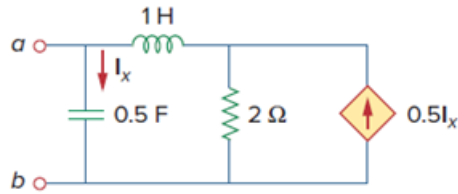


Problem

(a) For the circuit in Fig. 14.97, draw the new circuit after it has been scaled by $K_m = 200$ and $K_f = 104$.

(b) Obtain the Thevenin equivalent impedance at terminals a - b of the scaled circuit at $\omega = 104$ rad/s.

Figure 14.97:



Step-by-step solution

Step 1 of 8

(a)

Refer to Figure 14.97 in the textbook.

Consider that the circuit is scaled by the following scaling factors:

$$K_m = 200$$

$$K_f = 10^4$$

Here, K_m is the magnitude scaling factor and K_f is the frequency scaling factor.

Find the new values of the circuit.

The new value of resistance is,

$$\begin{aligned} R' &= K_m R \\ &= (200)(2) \\ &= 400 \, \Omega \end{aligned}$$

The new value of inductance is,


$$\begin{aligned} L' &= \frac{K_m}{K_f} L \\ &= \left(\frac{200}{10^4} \right) (1) \\ &= 0.02 \, \text{H} \end{aligned}$$

The new value of capacitance is,

$$\begin{aligned} C' &= \frac{1}{K_m K_f} C \\ &= \frac{0.5}{(200)(10^4)} \\ &= 0.25 \, \mu\text{F} \end{aligned}$$

Step 2 of 8

The new circuit after scaling is,

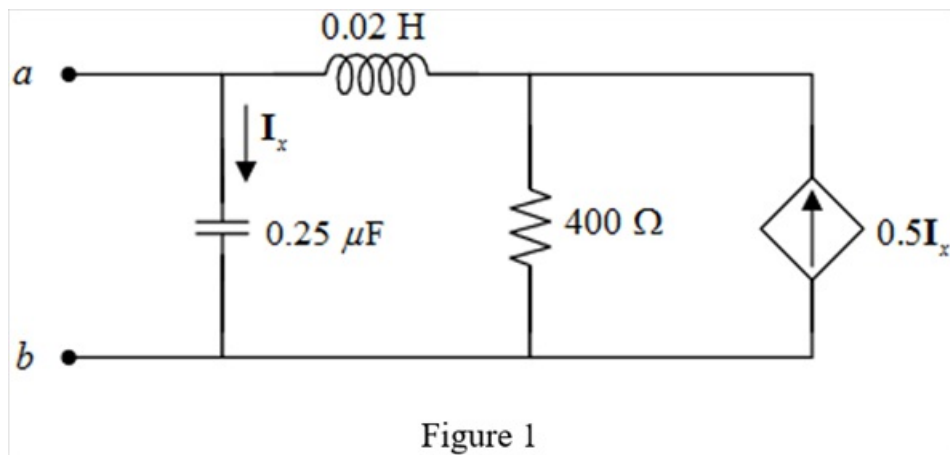

Step 3 of 8

(b)

Consider that the circuit operates at the angular frequency $\omega = 10^4$ rad/s.

Calculate the values of circuit elements in frequency domain.

$$R' = 400 \, \Omega$$

$$X'_L = j\omega L'$$

$$= j(10^4)(0.02)$$

$$= j200 \, \Omega$$

$$X'_C = \frac{1}{j\omega C'}$$


$$= \frac{1}{j(10^4)(0.25 \times 10^{-6})}$$

$$= \frac{1}{j0.0025}$$

$$= -j400 \, \Omega$$

Step 4 of 8

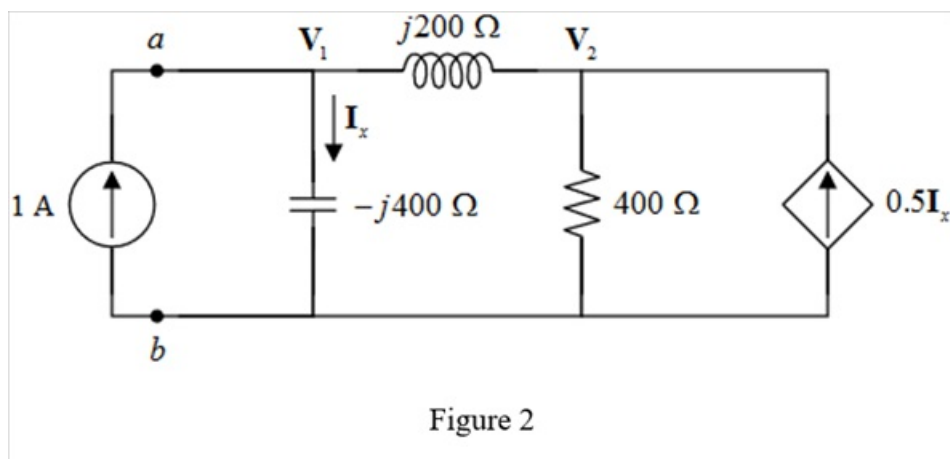Apply a 1 A current source between the terminals of a and b and convert the circuit in to frequency domain.



Step 5 of 8

Apply Kirchhoff's current law both the nodes in the circuit.

The node equation at V_1 is,

$$1 \text{ A} = \frac{V_1}{-j400} + \frac{V_1 - V_2}{j200}$$

Simplify the equation.

$$1 = V_1 \left(\frac{1}{-j400} + \frac{1}{j200} \right) - V_2 \frac{1}{j200}$$

$$V_1 (j0.0025 - j0.005) - V_2 (-j0.005) = 1$$

$$V_1 (-j0.0025) - 1 = V_2 (-j0.005)$$

$$\begin{aligned} V_2 &= \frac{V_1 (-j0.0025) - 1}{-j0.005} \\ &= \frac{V_1}{2} - j200 \end{aligned}$$

Step 6 of 8

The node equation at V_2 is,

$$\frac{V_2 - V_1}{j200} + \frac{V_2}{400} = 0.5I_x$$

Here, the current I_x in the circuit is,

$$I_x = \frac{V_1}{-j400}$$

Therefore,

$$\frac{V_2 - V_1}{j200} + \frac{V_2}{400} = 0.5 \left(\frac{V_1}{-j400} \right)$$

Simplify the equation.

$$V_2 \left(\frac{1}{j200} + \frac{1}{400} \right) - \frac{V_1}{j200} = V_1 \left(\frac{0.5}{-j400} \right)$$

$$V_2 \left(\frac{1}{j200} + \frac{1}{400} \right) = V_1 \left(\frac{0.5}{-j400} + \frac{1}{j200} \right)$$

$$V_2 (-j0.005 + 0.0025) = V_1 \left(\frac{1.5}{j400} \right)$$

Step 7 of 8

Simplify the equation further to get the expression of V_1 .

$$\begin{aligned} V_1 &= \frac{V_2(-j0.005 + 0.0025)(j400)}{1.5} \\ &= \left(\frac{2 + j1}{1.5}\right)V_2 \\ &= (1.34 + j0.67)V_2 \end{aligned}$$

Substitute the expression of V_2 .

$$\begin{aligned} V_1 &= (1.34 + j0.67)\left(\frac{V_1}{2} - j200\right) \\ &= (0.67 + j0.34)V_1 - (-133.34 + j266.67) \end{aligned}$$

Simplify the equation further to get the value of V_1 .

$$\begin{aligned} V_1 - (0.67 + j0.34)V_1 &= -(-133.34 + j266.67) \\ (0.34 - j0.34)V_1 &= 133.34 - j266.67 \\ V_1 &= \frac{133.34 - j266.67}{0.34 - j0.34} \\ &\approx 600 - j200 \\ &= 632.45 \angle -18.435^\circ \text{ V} \end{aligned}$$

Step 8 of 8

Calculate the Thevenin's equivalent impedance of the circuit seen through the terminals a and b .

$$\begin{aligned} Z_{th} &= \frac{V_1}{I} \\ &= \frac{632.45 \angle -18.435^\circ}{1} \\ &= 632.45 \angle -18.435^\circ \Omega \end{aligned}$$

Thus, the Thevenin's equivalent impedance of the circuit seen through the terminals a and b is $\boxed{632.45 \angle -18.435^\circ \Omega}$.