

Problem

The circuit shown in Fig. 14.98 has the impedance


$$Z(s) = \frac{1,000(s+1)}{(s+1+j50)(s+1-j50)}, \quad s = j\omega$$

Find:

(a) the values of R , L , C , and G

(b) the element values that will raise the resonant frequency by a factor of 103 by frequency scaling

Figure 14.98:

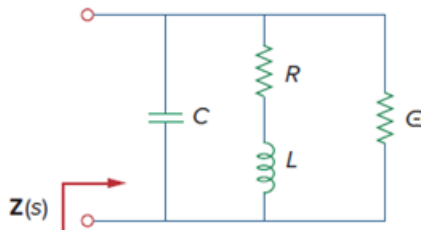

Step-by-step solution

Step 1 of 2

$$(a) \quad \frac{1}{Z} = G + j\omega C + \frac{1}{R + j\omega L} = \frac{(G + j\omega C)(R + j\omega L) + 1}{R + j\omega L}$$

$$\text{which leads to } Z = \frac{j\omega L + R}{-\omega^2 LC + j\omega(RC + LG) + GR + 1}$$

$$Z(\omega) = \frac{j\frac{\omega}{C} + \frac{R}{LC}}{-\omega^2 + j\omega\left(\frac{R}{L} + \frac{G}{C}\right) + \frac{GR+1}{LC}} \quad (1)$$

$$\text{We compare this with the given impedance } Z(\omega) = \frac{1000(j\omega+1)}{-\omega^2 + 2j\omega + 1 + 2500} \quad (2)$$

comparing (1) and (2) shows that

$$\frac{1}{C} = 1000 \rightarrow C = 1\text{mF}, \quad \frac{R}{L} = 1 \rightarrow R = L$$

$$\frac{R}{L} = \frac{G}{C} = 2 \rightarrow G = C = 1\text{ms}$$

$$2501 = \frac{GR+1}{LC} = \frac{10^{-3}R+1}{10^{-3}R} \rightarrow R = L = 0.4$$

thus, $R = 0.4\Omega$, $L = 0.4\text{H}$, $C = 1\text{mF}$, $G = 1\text{ms}$

Step 2 of 2

(b) By frequency - scaling, $K_f = 1000$

$$R' = 0.4\Omega, \quad G = 1ms$$

$$L' = \frac{L}{K_f} = \frac{0.4}{10^3} = 0.4MH_z$$

$$C' = \frac{C}{K_f} = \frac{10^{-3}}{10^{-3}} = 1\mu F$$