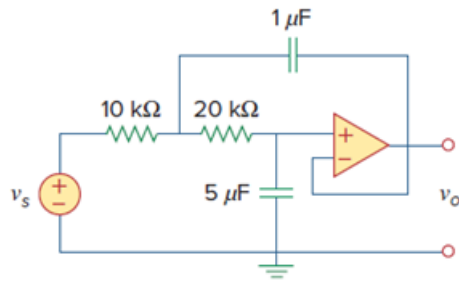


Problem

The op amp circuit in Fig. 14.100 is to be magnitude-scaled by 100 and frequency-scaled by 105. Find the resulting element values.

Figure 14.100:



Step-by-step solution

Step 1 of 1

$$1\mu F \rightarrow C' = \frac{1}{K_m K_f} C = \frac{10^{-6}}{100 \times 10^5} = 0.1 PF$$

$$5\mu F \rightarrow C' = 0.5 PF$$

$$10K\Omega \rightarrow A' = K_m R = 100 \times 10 K\Omega = 1M\Omega$$

$$20K\Omega \rightarrow R' = 2M\Omega$$