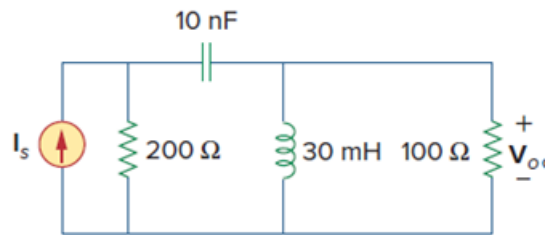


Problem

Use *PSpice* or *MultiSim* to obtain the magnitude and phase plots of V_o of the circuit in Fig. 14.102.

Figure 14.102:



Step-by-step solution

Step 1 of 4

Refer to circuit diagram in Figure 14.102 in the textbook.

PSpice simulation:

The schematic circuit is shown in Figure 1.

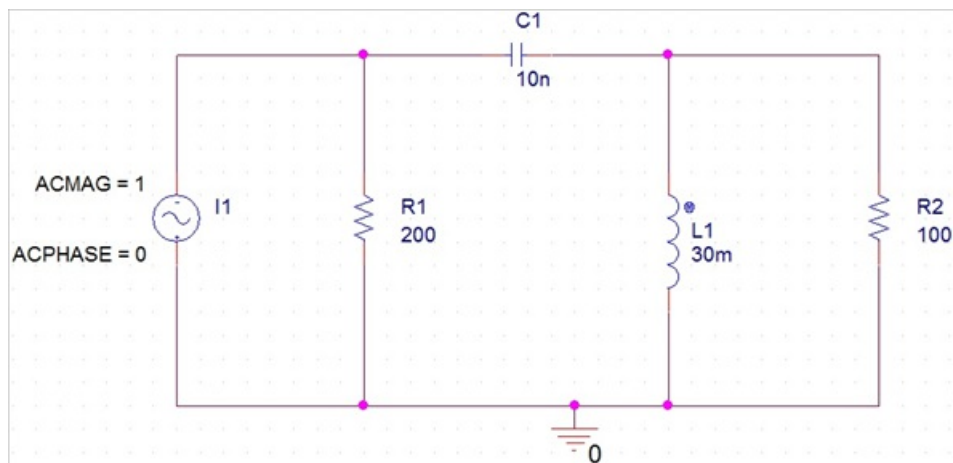


Figure 1

Step 2 of 4

Simulation settings window is shown in Figure 2.

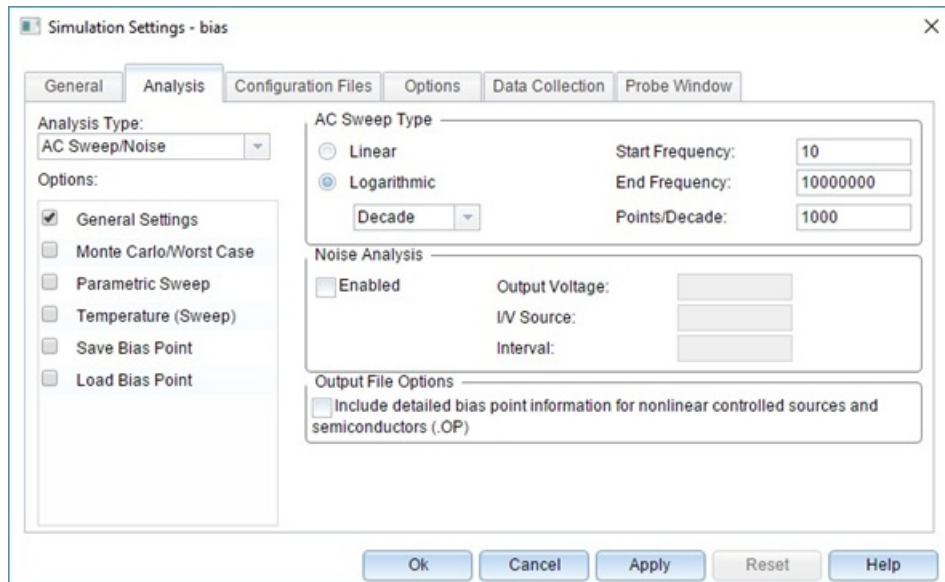


Figure 2

Step 3 of 4

The magnitude plot of V_o/I_s is shown in Figure 3.

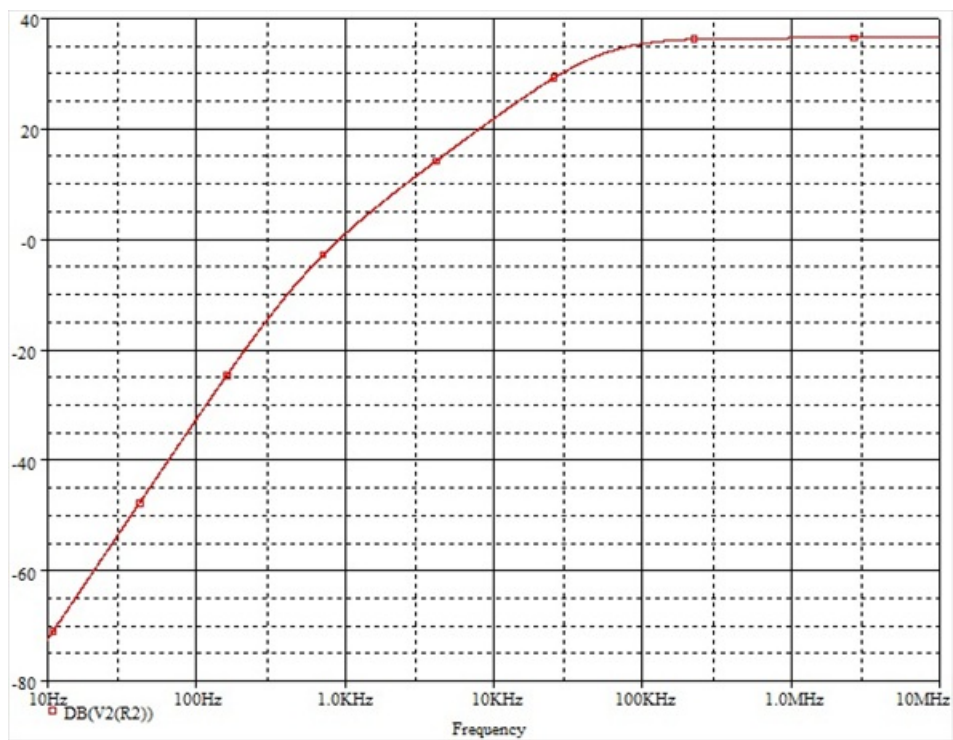


Figure 3

Therefore, the magnitude plot of V_o/I_s is shown in Figure 3.

Step 4 of 4

The phase plot of $\frac{V_o}{I_s}$ is shown in Figure 4.

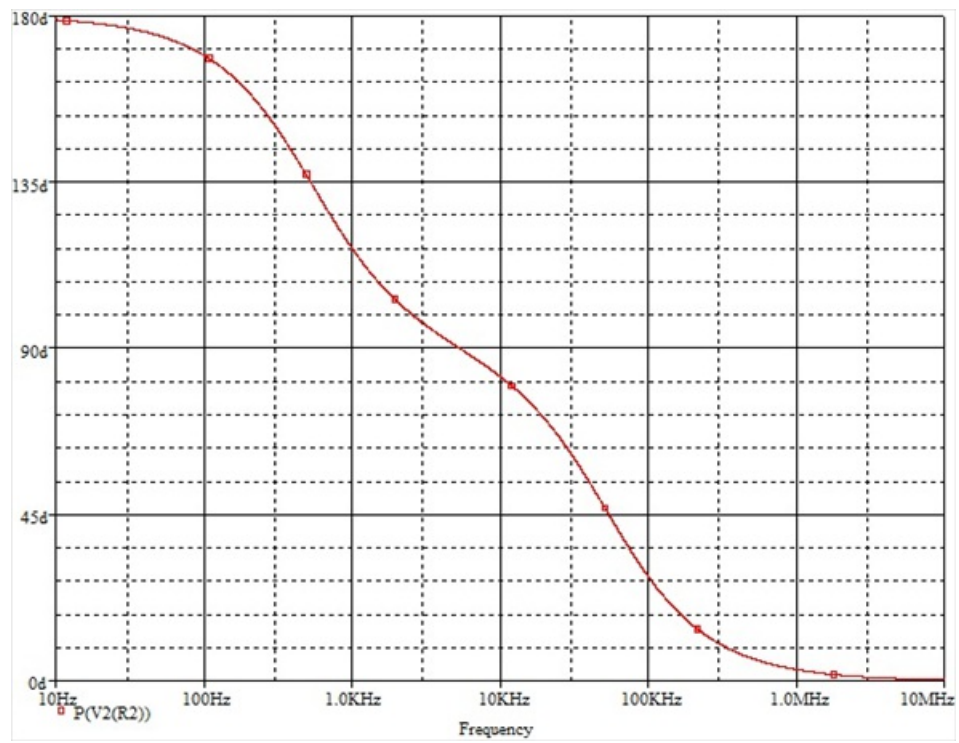


Figure 4

Therefore, the phase plot of $\frac{V_o}{I_s}$ is shown in Figure 4.