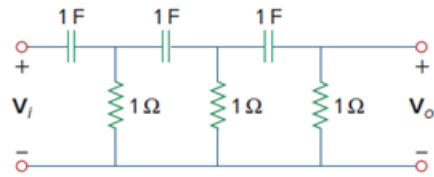


Problem

In the interval $0.1 < f < 100$ Hz, plot the response of the network in Fig. 14.104. Classify this filter and obtain ω_0 .

Figure 14.104:




Step-by-step solution

Step 1 of 3

The schematic is shown below. In the A.C sweep box, we set total points = 50, start frequency = 1, and end frequency = 100, after simulation, we obtain the magnitude response as shown below.

It is evident from the response that the circuit represents a high pass filter

Step 2 of 3

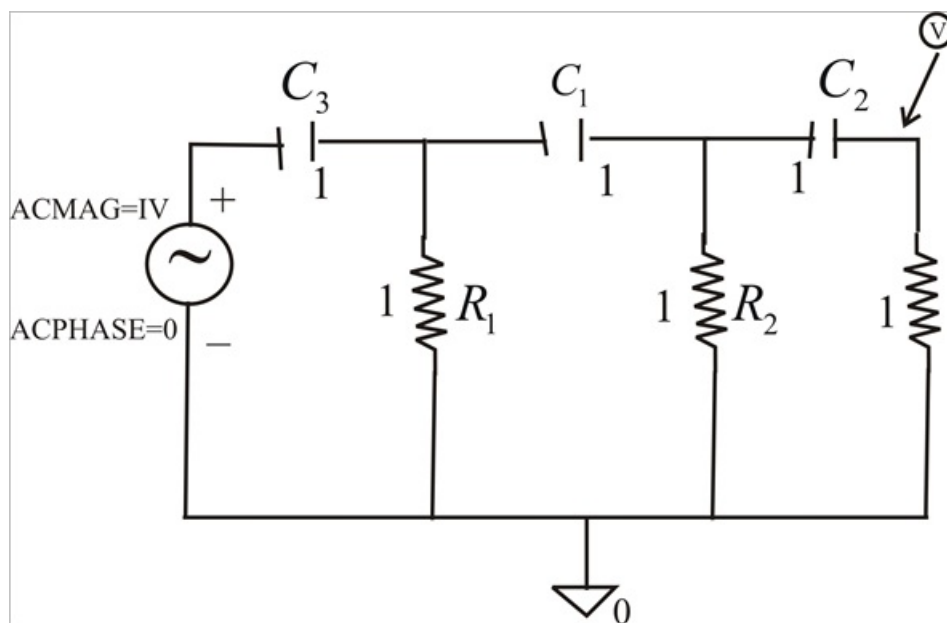

Step 3 of 3

