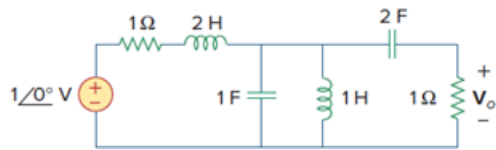


Problem

Use *PSpice* or *MultiSim* to generate the magnitude and phase Bode plots of V_o in the circuit of Fig. 14.105.

Figure 14.105:




Step-by-step solution

Step 1 of 3

The schematic is shown below. We insert a voltage marker to measure V_o . In the A.C sweep box, we set total points = 101, start frequency = 1, and end frequency = 100. After simulation, we obtain the magnitude and phase plots of V_o as shown below.

Step 2 of 3

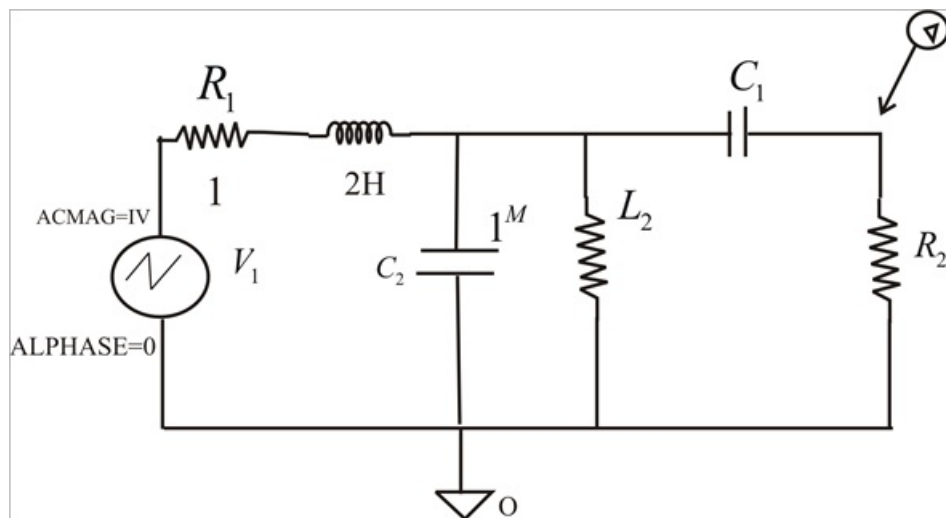

Step 3 of 3

