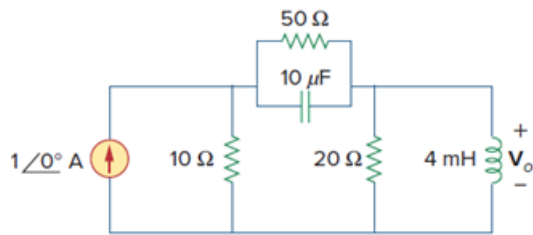


Problem

Obtain the magnitude plot of the response V_o in the network of Fig. 14.106 for the frequency interval $100 < f < 1,000$ Hz.

Figure 14.106:




Step-by-step solution

Step 1 of 3

The schematic is shown below. In the A.C sweep box, we type total points = 101, start frequency = 100, end frequency = 1 K. After simulation, the magnitude plots of the response V_o , is obtained as shown below.

Step 2 of 3

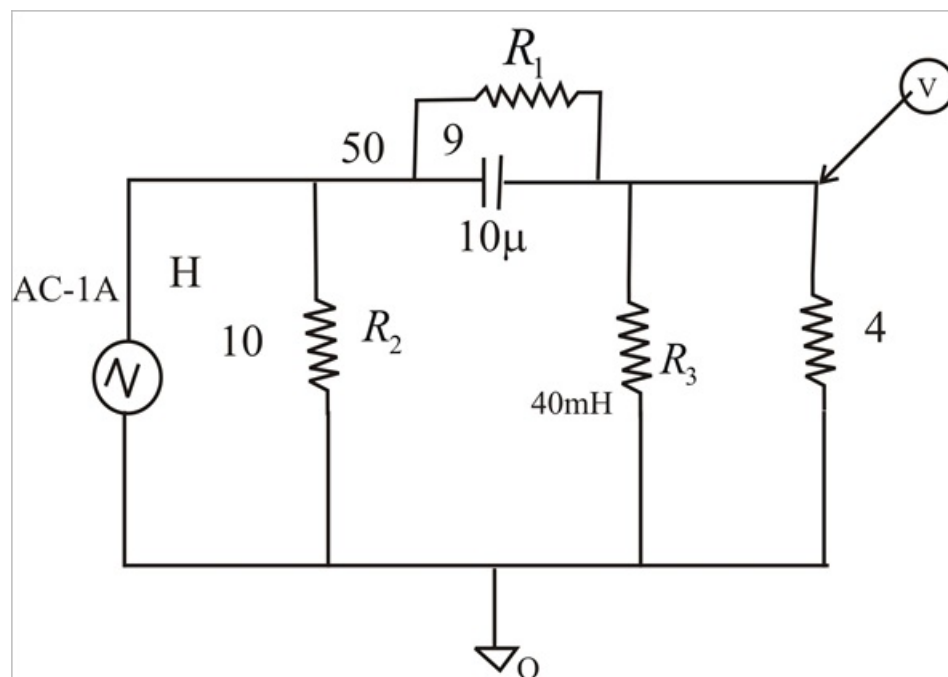

Step 3 of 3

