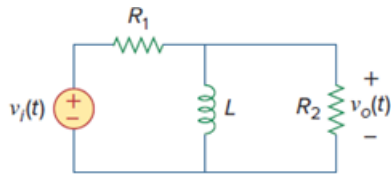


Problem

Obtain the frequency response of the circuit in Fig. 14.40 (see Practice Problem 14.10). Take $R_1 = R_2 = 100\ \Omega$, $L = 2\text{ mH}$. Use $1 < f < 100,000\text{ Hz}$.

Figure 14.40:




Step-by-step solution

Step 1 of 3

The schematic is shown below. In the A.C sweep box, we set total points = 1001, start frequency = 1 and end frequency = 100 K. After simulation, we obtain the magnitude plot of the response as shown below. The response shows that the circuit is a HPF.

Step 2 of 3

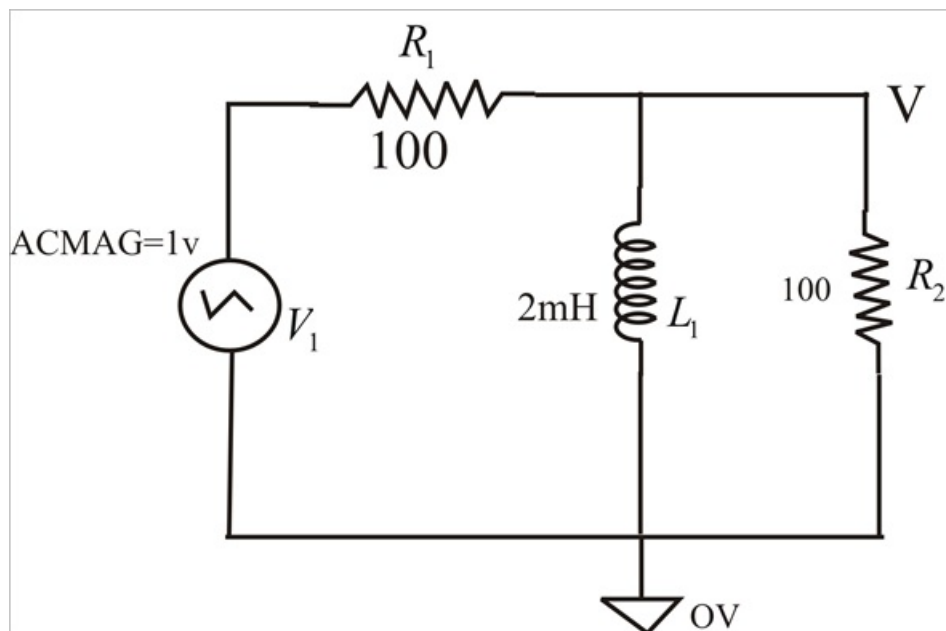

Step 3 of 3

