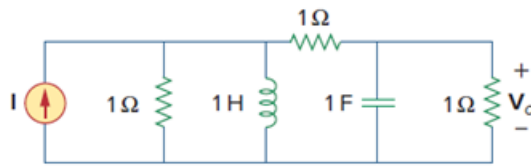


Problem

Using *PSpice* or *MultiSim*, plot the magnitude of the frequency response of the circuit in Fig. 14.85.

Figure 14.85:




Step-by-step solution

Step 1 of 3

The schematic is shown below. We type total points = 101, start frequency = 1, and end frequency = 100 in the A.C sweep box. After simulation the circuit the magnitude plot of the frequency response is shown below.

Step 2 of 3

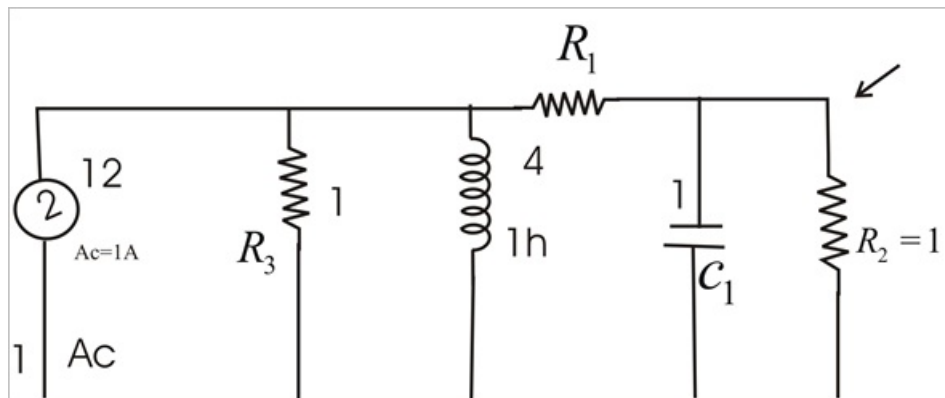

Step 3 of 3

