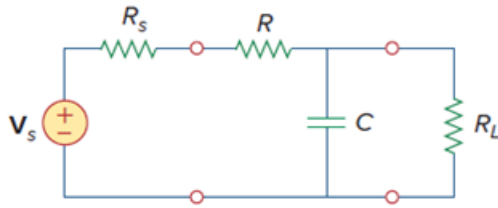


Problem

Practical RC filter design should allow for source and load resistances as shown in Fig. 14.110. Let $R = 4\text{ k}\Omega$ and $C = 40\text{-nF}$. Obtain the cutoff frequency when:

(a) $R_s = 0$, $R_L = \infty$,

(b) $R_s = 1\text{ k}\Omega$, $R_L = 5\text{ k}\Omega$.



Step-by-step solution

Step 1 of 2

(a) When $R_s = 0$ and $R_L = \infty$, we have a Low pass filter

$$\omega_c = 2\pi fC = \frac{1}{RC}$$

$$fC = \frac{1}{2\pi RC} = \frac{1}{(2\pi)(4 \times 10^3)(40 \times 10^{-9})}$$

$$= 994.7\text{ Hz}$$

Step 2 of 2

(b) We obtain R_{TH} across the capacitor

$$R_{TH} = R_L \parallel (R + R_s)$$

$$R_{TH} = 5 \parallel (4 + 1) = 2.5\text{ k}\Omega$$

$$fC = \frac{1}{2\pi R_{TH} C} = \frac{1}{(2\pi)(2.5 \times 10^3)(40 \times 10^{-9})}$$

$$fC = 1.59\text{ kHz}$$