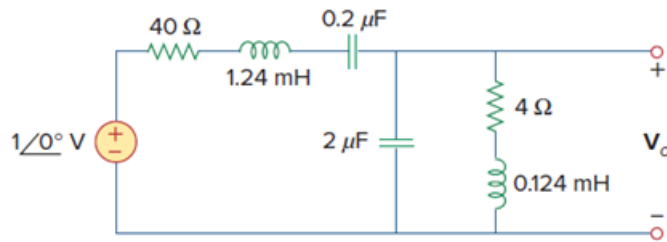


Problem

A low-quality-factor, double-tuned band-pass filter is shown in Fig. 14.112. Use *PSpice* or *MultiSim* to generate the magnitude plot of $V_o(\omega)$.

Figure 14.112:




Step-by-step solution

Step 1 of 3

The schematic is shown below. We click Analysis / Setup / AC sweep and enter total points = 1001, start frequency = 100, and end frequency = 100 K.

After simulation, we obtain the magnitude plot of the response as shown

Step 2 of 3

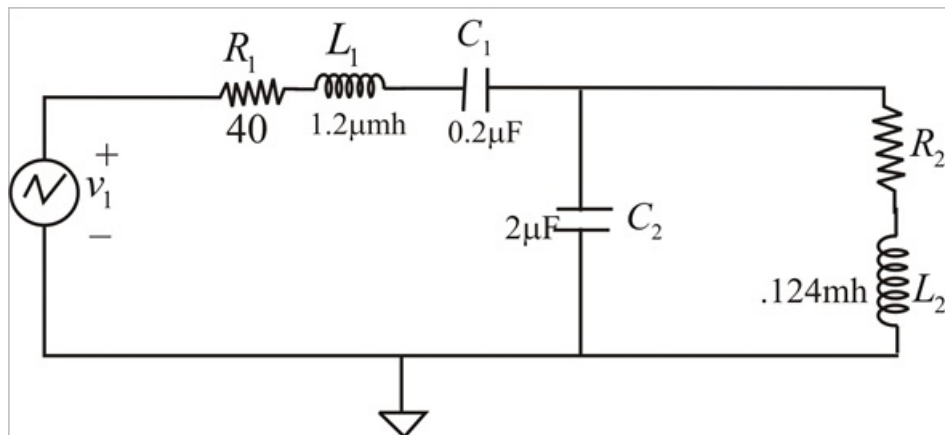

Step 3 of 3

