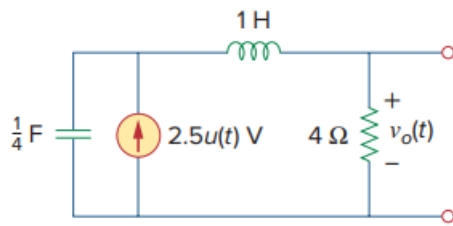


Problem

Determine $v_o(t)$ in the circuit of Fig. 16.6, assuming zero initial conditions.

Figure 16.6:



Step-by-step solution

Step 1 of 4

Refer to the circuit in Figure 16.6 in the textbook.


Transform the circuit to the s -domain.

$$2.5u(t) \Rightarrow \frac{2.5}{s}$$

$$\frac{1}{4} \text{ F} \Rightarrow \frac{1}{sC} = \frac{4}{s}$$

$$1 \text{ H} \Rightarrow sL = s$$

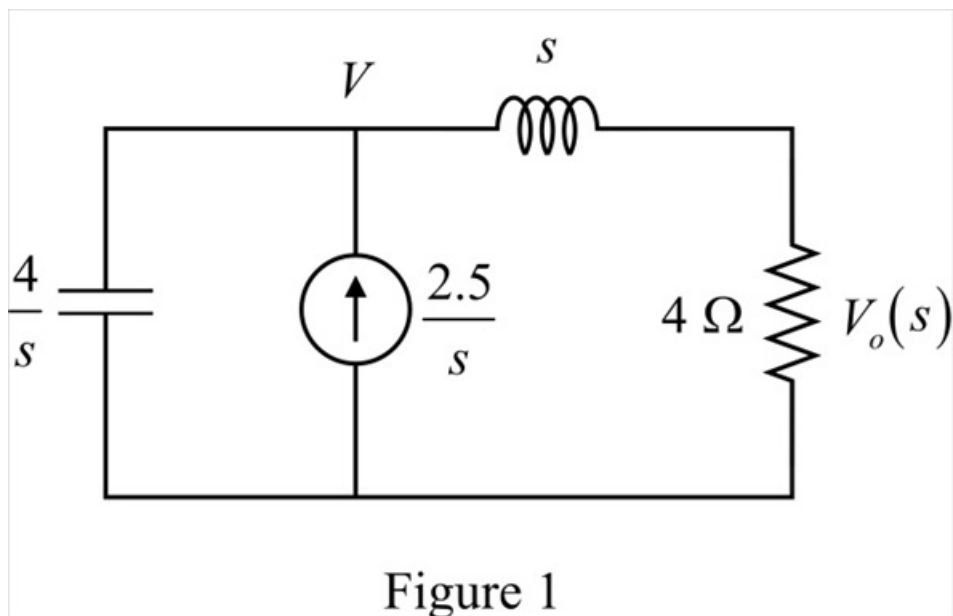Draw the modified circuit as shown in Figure 1.



Step 2 of 4

Apply current division principle and ohm's law to calculate the voltage $V_o(s)$.

$$\begin{aligned} V_o(s) &= \left[\frac{2.5}{s} \times \frac{\frac{4}{s}}{\left(\frac{4}{s} + s + 4\right)} \right] (4) \\ &= \frac{40s}{s^2(s^2 + 4s + 4)} \\ &= \frac{40}{s(s^2 + 4s + 4)} \\ &= \frac{40}{s(s+2)^2} \end{aligned}$$

$$V_o(s) = \frac{A}{S} + \frac{B}{S+2} + \frac{C}{(S+2)^2} \dots\dots (1)$$

$$40 = A(S+2)^2 + BS(S+2) + CS$$

$$A(S^2 + 4S + 4) + B(S^2 + 2S) + CS = 40$$

$$S^2(A+B) + S(4A+2B+C) + 4A = 40$$

Step 3 of 4

By comparing constant coefficients,

$$4A = 40$$

$$A = 10$$

By comparing s^2 coefficients,

$$A + B = 0$$

$$B = -10$$

By comparing s coefficients,

$$4A + 2B + C = 0$$

$$C = -20$$

Step 4 of 4

Substitute 10 for A, -10 for B, and -20 for C in equation (1).

$$V_o(s) = \frac{10}{S} - \frac{10}{S+2} - \frac{20}{(S+2)^2}$$

Apply inverse Laplace transform.

$$\begin{aligned} v_o(t) &= 10u(t) - 10e^{-2t}u(t) - 20te^{-2t}u(t) \\ &= [10 - 10e^{-2t} - 20te^{-2t}]u(t) \text{ V} \end{aligned}$$

Thus, the voltage $v_o(t)$ is $\boxed{10[1 - e^{-2t} - 2te^{-2t}]u(t) \text{ V}}$.