

Chapter 16, Problem 1RQ

Problem

The voltage through a resistor with current $i(t)$ in the s -domain is $sRI(s)$.

- (a) True
- (b) False

Step-by-step solution

Step 1 of 1

- (b) "R I (S)
FALSE