

Problem

The current through an RL series circuit with input voltage $v(t)$ is given in the s -domain as:

(a) $V(s) \left[R + \frac{1}{sL} \right]$

(b) $V(s)(R + sL)$

(c) $\frac{V(s)}{R + 1/sL}$

(d) $\frac{V(s)}{R + sL}$

Step-by-step solution

Step 1 of 1

$$v(t) = \frac{V(s)}{R + sL}$$

(d)