

Problem

The impedance of a 10-F capacitor is:

- (a) $10/s$
- (b) $s/10$
- (c) $1/10s$
- (d) $10s$

Step-by-step solution

Step 1 of 1

Impedance of a 10F capacitor is given by

$$\frac{1}{10s}$$

(C)