

Problem

The step responses of a series RLC circuit are

$$V_c = 40 - 10e^{-2000t} - 10e^{-4000t} \text{ V}, t > 0$$

$$i_L(t) = 3e^{-2000t} + 6e^{-4000t} \text{ mA}, t > 0$$

(a) Find C .

(b) Determine what type of damping is exhibited by the circuit.

Step-by-step solution

Step 1 of 4

Consider the responses of series RLC circuit is

$$i_L(t) = (3e^{-2000t} + 6e^{-4000t}) \text{ mA}$$

$$v_c(t) = (40 - 10e^{-2000t} - 10e^{-4000t}) \text{ V}$$

Draw the series RLC circuit.

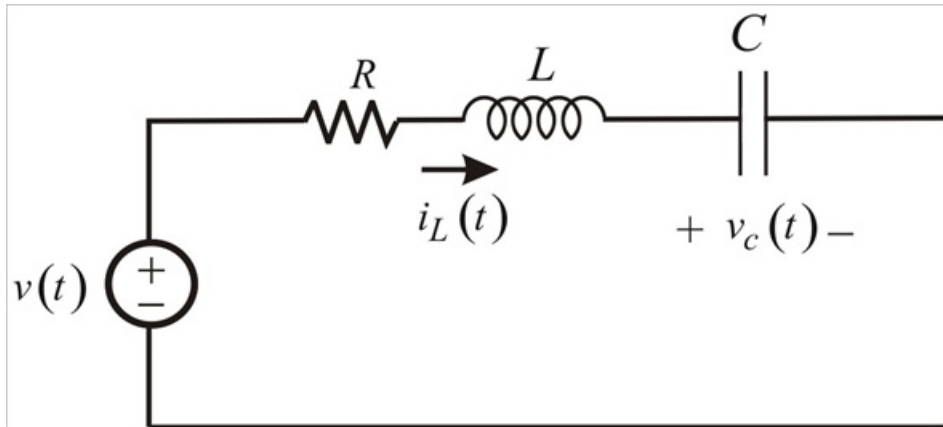


Figure 1: Series RLC circuit

Step 2 of 4

(a)

In series RLC circuit same current flows through the each element. So,

$$i_L(t) = i_c(t)$$

$$i_L(t) = C \frac{dv_c(t)}{dt}$$

$$(3e^{-2000t} + 6e^{-4000t}) \times 10^{-3} = C \frac{d}{dt} (40 - 10e^{-2000t} - 10e^{-4000t})$$

$$(3e^{-2000t} + 6e^{-4000t}) \times 10^{-3} = C (2 \times 10^4 e^{-2000t} + 4 \times 10^4 e^{-4000t})$$

Compare the exponential terms.

$$3 \times 10^{-3} = 2 \times 10^4 C$$

$$C = 0.15 \times 10^{-6}$$

$$C = 0.15 \mu\text{F}$$

Thus, the capacitor value is $\boxed{0.15 \mu\text{F}}$.

(b)

Write the Laplace transform pairs those are used to find $I_L(s)$.

$$u(t) \xleftrightarrow{\mathcal{L}} \frac{1}{s}$$

$$e^{-at}u(t) \xleftrightarrow{\mathcal{L}} \frac{1}{s+a}$$

Calculate the Laplace transform of $i_L(t)$.

$$\begin{aligned} I_L(s) &= \left(\frac{3}{s+2000} + \frac{6}{s+4000} \right) 10^{-3} \\ &= \left[\frac{3(s+4000) + 6(s+2000)}{(s+2000)(s+4000)} \right] 10^{-3} \\ &= \left[\frac{9s + 24000}{(s+2000)(s+4000)} \right] 10^{-3} \\ &= \left[\frac{9s + 24000}{s^2 + 6000s + 8 \times 10^6} \right] 10^{-3} \end{aligned}$$

Step 4 of 4

Characteristic equation of $I_L(s)$.

$$s^2 + 6000s + 8 \times 10^6 = 0$$

Compare the characteristic equation $s^2 + 6000s + 8 \times 10^6 = 0$ with the standard equation

$$s^2 + 2\zeta\omega_n s + \omega_n^2 = 0.$$

$$\omega_n^2 = 8 \times 10^6$$

$$2\zeta\omega_n = 6000$$

$$\omega_n = 2.828 \times 10^3$$

$$2\zeta \left((2.828)(10^3) \right) = 6000$$

$$\zeta = \frac{6000}{(2)(2.828)(10^3)}$$

$$\zeta = 1.06$$

The damping value is greater than 1 ($\zeta > 1$). So, the system is over damped system.