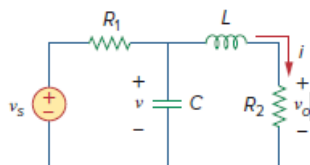


Problem

Obtain the state variable model for the circuit shown in Fig. 16.23. Let $R_1 = 1$, $R_2 = 2$, $C = 0.5$, and $L = 0.2$ and obtain the transfer function.


Figure 16.23:



Step-by-step solution

Step 1 of 5

Given circuit

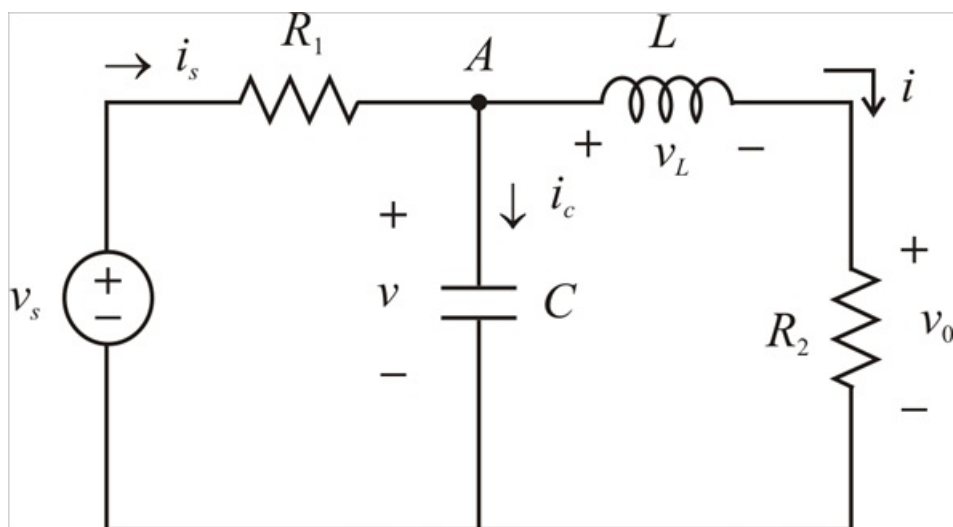

Step 2 of 5

Consider the inductor current i and capacitor voltage v as the state variables.

$$v_L = L \frac{di}{dt}$$

$$i_c = C \frac{dv}{dt}$$

Applying KCL at node A gives

$$i_s = i_c + i$$

$$\frac{v_s - v}{R_1} = C \frac{dv}{dt} + i$$

$$C \frac{dv}{dt} = \frac{v_L}{R_1} - \frac{v}{R_1} - i$$

$$\dot{v} = \frac{v_s}{R_1 C} - \frac{v}{R_1 C} - \frac{i}{C} \quad \text{---(1)}$$

Step 3 of 5

Applying KVL around the second inner loop, we get

$$-v + v_L + v_0 = 0$$

$$v - v_0 = v_L$$

$$v - v_0 = v_L$$

$$L \frac{di}{dt} = v - iR_2$$

$$\dot{i} = \frac{v}{L} - \frac{iR_2}{L} \quad \text{---(2)}$$

And

$$v_0 = iR_2$$

From equations (1) and (2) we can constitute the state equations. the output voltage

$$v_0 = iR_2 \quad \text{---(3)}$$

$$\begin{bmatrix} \dot{v} \\ \dot{i} \end{bmatrix} = \begin{bmatrix} \frac{-1}{R_1 C} & \frac{-1}{C} \\ \frac{1}{L} & \frac{-R_2}{L} \end{bmatrix} \begin{bmatrix} v \\ i \end{bmatrix} + \begin{bmatrix} \frac{1}{R_1 C} \\ 0 \end{bmatrix} v_s \quad \text{---(4)}$$

$$v_0 = \begin{bmatrix} 0 & R_2 \end{bmatrix} \begin{bmatrix} v \\ i \end{bmatrix} \quad \text{---(5)}$$

Step 4 of 5

Given $R_1 = 1, R_2 = 2, C = 0.5$ and $L = 0.2$ Substituting in equation (4) and (5), where the matrices are

$$A = \begin{bmatrix} \frac{-1}{R_1 C} & \frac{-1}{C} \\ \frac{1}{L} & \frac{-R_2}{L} \end{bmatrix}$$

$$A = \begin{bmatrix} \frac{-1}{(1)(0.5)} & \frac{-1}{0.5} \\ \frac{1}{0.2} & \frac{-2}{0.2} \end{bmatrix}$$

$$A = \begin{bmatrix} -2 & -2 \\ 5 & -10 \end{bmatrix}$$

$$B = \begin{bmatrix} \frac{1}{R_1 C} \\ 0 \end{bmatrix}$$

$$B = \begin{bmatrix} \frac{1}{(1)(0.5)} \\ 0 \end{bmatrix}$$

$$B = \begin{bmatrix} 2 \\ 0 \end{bmatrix}$$

Step 5 of 5

$$C = [0 \quad R_2]$$

$$C = [0 \quad 2]$$

$$sI - A = \begin{bmatrix} s & 0 \\ 0 & s \end{bmatrix} - \begin{bmatrix} -2 & -2 \\ 5 & -10 \end{bmatrix}$$

$$sI - A = \begin{bmatrix} s+2 & 2 \\ -5 & s+10 \end{bmatrix}$$

The inverse of the above matrices is

$$(sI - A)^{-1} = \frac{\text{adjoint of } A}{\text{determinant of } A}$$

$$(sI - A)^{-1} = \frac{\begin{bmatrix} s+10 & -2 \\ +5 & s+2 \end{bmatrix}}{s^2 + 12s + 20 + 10}$$

$$(sI - A)^{-1} = \frac{\begin{bmatrix} s+10 & -2 \\ +5 & s+2 \end{bmatrix}}{s^2 + 12s + 30}$$

Thus, the transfer function is given by

$$H(s) = C(sI - A)^{-1} B$$

$$H(s) = \frac{\begin{bmatrix} 0 & 2 \end{bmatrix} \begin{bmatrix} s+10 & -2 \\ +5 & s+2 \end{bmatrix} \begin{bmatrix} 2 \\ 0 \end{bmatrix}}{s^2 + 12s + 30}$$

$$H(s) = \frac{\begin{bmatrix} 0 & 2 \end{bmatrix} \begin{bmatrix} 2s+20 \\ +10 \end{bmatrix}}{s^2 + 12s + 30}$$

$$\therefore H(s) = \frac{20}{s^2 + 12s + 30}$$