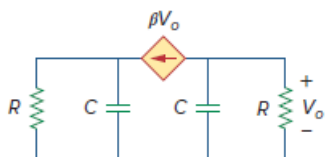


Problem

For what value of β is the circuit in Fig. 16.29 stable?


Figure 16.29:



Step-by-step solution

Step 1 of 6

The circuit in s-domain

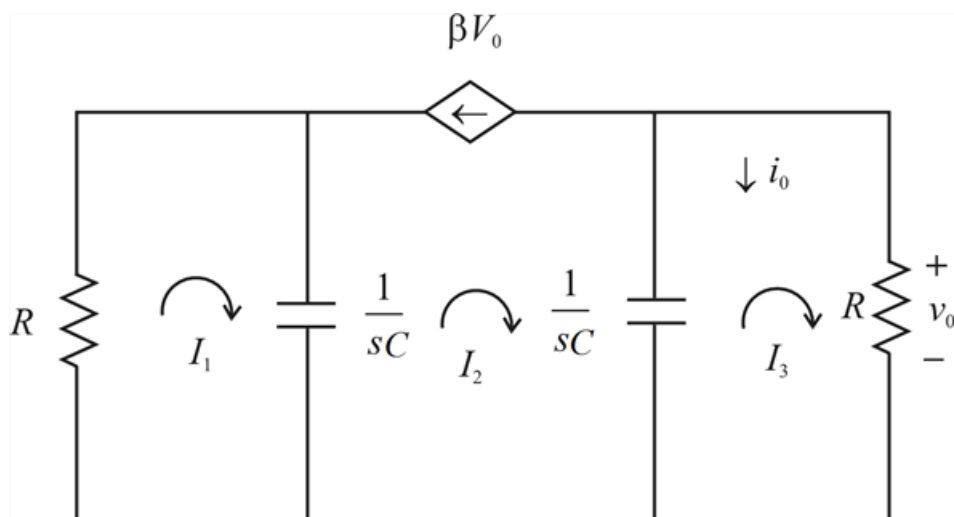

Step 2 of 6

Applying mesh analysis to the first-order circuit at loop (1)

$$I_1 R + \frac{1}{sC}(I_1 - I_2) = 0$$

$$I_1 \left(R + \frac{1}{sC} \right) - \frac{1}{sC} = 0 \quad \text{---(1)}$$

At loop (2)

We know that

$$V_o = I_3 R$$

$$I_2 = -\beta V_o$$

$$I_2 = -\beta R I_3$$

$$I_2 + \beta R I_3 = 0 \quad \text{---(2)}$$

At loop (3)

$$\frac{1}{sC}(I_3 - I_2) + R I_3 = 0$$

$$I_3 \left(R + \frac{1}{sC} \right) - \frac{1}{sC} I_2 = 0 \quad \text{---(3)}$$

Step 3 of 6

We can write equation (1), (2) and (3) in matrix form as

$$\begin{bmatrix} R + \frac{1}{sC} & \frac{-1}{sC} & 0 \\ 0 & 1 & \beta R \\ 0 & \frac{-1}{sC} & R + \frac{1}{sC} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

The determinant is

$$\Delta = \left(R + \frac{1}{sC} \right) \left\{ R + \frac{1}{sC} + \frac{\beta R}{sC} \right\} + \frac{1}{sC} \{0 - 0\} + 0$$

$$\Delta = \left(R + \frac{1}{sC} \right)^2 + \frac{\beta R^2}{sC} + \frac{\beta R}{s^2 C^2}$$

$$\Delta = R^2 + \frac{1}{s^2 C^2} + \frac{2R}{sC} + \frac{\beta R^2}{sC} + \frac{\beta R}{s^2 C^2}$$

$$\Delta = \frac{R^2 s^2 C^2 + 2RsC + \beta R^2 sC + \beta R + 1}{s^2 C^2}$$

$$\Delta = \frac{s^2 (R^2 C^2) + s(2RC + \beta R^2 C) + \beta R + 1}{s^2 C^2}$$

Step 4 of 6

The characteristics equation ($\Delta = 0$) gives the poles as

$$s^2 (R^2 C^2) + s(2RC + \beta R^2 C) + \beta R + 1 = 0$$

$$P_{1,2} = \frac{-(2RC + \beta R^2 C) \pm \sqrt{(2RC + \beta R^2 C)^2 - 4(\beta R + 1)(R^2 C^2)}}{2R^2 C^2}$$

$$P_{1,2} = \frac{-(2RC + \beta R^2 C) \pm \sqrt{4R^2 C^2 + 4\beta R^3 C^2 + \beta^2 R^4 C^2 - 4\beta R^3 C^2 - 4R^2 C^2}}{2R^2 C^2}$$

$$P_{1,2} = \frac{-(2RC + \beta R^2 C) \pm \beta R^2 C}{2R^2 C^2}$$

Step 5 of 6

$$P_1 = \frac{-2RC - \beta R^2 C - \beta R^2 C}{2R^2 C^2}$$

$$P_2 = \frac{-2RC - \beta R^2 C + \beta R^2 C}{2R^2 C^2}$$

$$P_1 = \frac{-2RC - 2\beta R^2 C}{2R^2 C^2}$$

$$P_2 = \frac{-1}{RC}$$

$$P_1 = \frac{-2RC(1 + \beta R)}{2R^2 C^2}$$

For circuit to be stable roots must be located left half of the s plane

$$\therefore \frac{-2RC(1 + \beta R)}{2R^2 C^2} < 0$$

$$1 + \beta R > 0$$

$$\beta > -\frac{1}{R}$$

Step 6 of 6

Which is negative when $\beta > -\frac{1}{R}$