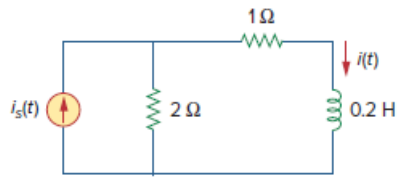


Problem

Find $i(t)$ for $t > 0$ for the circuit in Fig. 16.37. Assume $i_s(t) = [6(t) + 3\delta(t)]\text{mA}$.

Figure 16.37:



Step-by-step solution

Step 1 of 6

Refer to Figure 16.37 in the textbook.

There is typo error in the expression of source current. The expression for the source current is,

$$i_s(t) = [6u(t) + 3\delta(t)] \text{ mA}$$

Apply Laplace transform on both sides.

$$I_s(s) = \frac{6 \times 10^{-3}}{s} + 3 \times 10^{-3}$$

The inductance in s-domain is,

$$\begin{aligned} Z_L &= sL \\ &= 0.2s \, \Omega \end{aligned}$$

Step 2 of 6

Draw the circuit in s-domain.

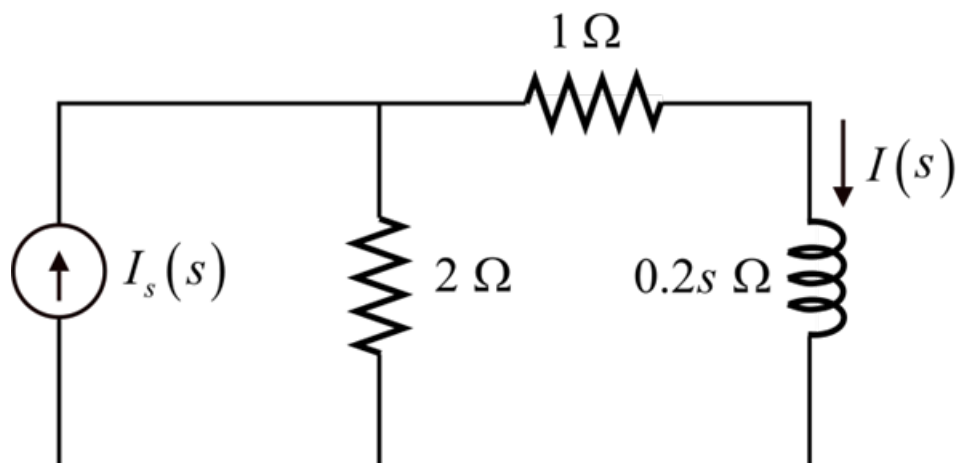


Figure 1

Step 3 of 6

Apply current division rule to calculate the expression for $I(s)$.

$$\begin{aligned}
 I(s) &= \left(\frac{2}{2+1+0.2s} \right) I_s(s) \\
 &= \left(\frac{2}{3+0.2s} \right) \left(\frac{6 \times 10^{-3}}{s} + 3 \times 10^{-3} \right) \\
 &= (10^{-3}) \left(\frac{10}{s+15} \right) \left(\frac{6}{s} + 3 \right) \\
 &= (10^{-3}) \left(\frac{10}{s+15} \right) \left(\frac{6+3s}{s} \right) \\
 &= (10^{-3}) \left(\frac{60+30s}{s(s+15)} \right)
 \end{aligned}$$

Step 4 of 6

Apply partial fractions to the function $\frac{60+30s}{s(s+15)}$.

$$\frac{60+30s}{s(s+15)} = \frac{A}{s} + \frac{B}{s+15}$$

Calculate the value of the unknown, A .

$$\begin{aligned}
 A &= s \left[\frac{60+30s}{s(s+15)} \right]_{s=0} \\
 &= \frac{60+30s}{(s+15)} \Big|_{s=0} \\
 &= \frac{60+0}{0+15} \\
 &= 4
 \end{aligned}$$

Step 5 of 6

Calculate the value of the unknown, B .

$$\begin{aligned}
 B &= (s+15) \left[\frac{60+30s}{s(s+15)} \right]_{s=-15} \\
 &= \frac{60+30s}{s} \Big|_{s=-15} \\
 &= \frac{60+30(-15)}{-15} \\
 &= 26
 \end{aligned}$$

Step 6 of 6

The expression for $I(s)$ is,

$$\begin{aligned} I(s) &= (10^{-3}) \left(\frac{60+30s}{s(s+15)} \right) \\ &= (10^{-3}) \left(\frac{4}{s} + \frac{26}{s+15} \right) \\ &= \frac{4 \times 10^{-3}}{s} + \frac{26 \times 10^{-3}}{s+15} \end{aligned}$$

Apply inverse Laplace transforms on both sides.

$$\begin{aligned} i(t) &= (4 \times 10^{-3}) u(t) + (26 \times 10^{-3}) e^{-15t} u(t) \\ &= (4 + 26e^{-15t}) u(t) \text{ mA} \end{aligned}$$

Thus, the expression for the output current is $\boxed{(4 + 26e^{-15t}) u(t) \text{ mA}}$.