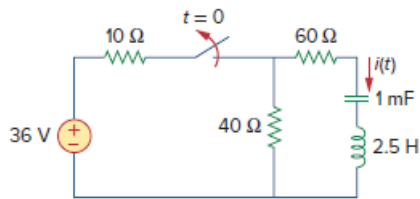


Problem

Find $i(t)$ for $t > 0$ in the circuit of Fig. 16.43.

Figure 16.43:



Step-by-step solution

Step 1 of 5

Refer to Figure 16.43 in the textbook.

The switch is initially closed for $t < 0$. So, the circuit remains in the steady state for $t < 0$ and the inductor and the capacitor are replaced by the short and open circuit respectively.

Redraw the circuit for $t = 0^-$ as shown in Figure 1.

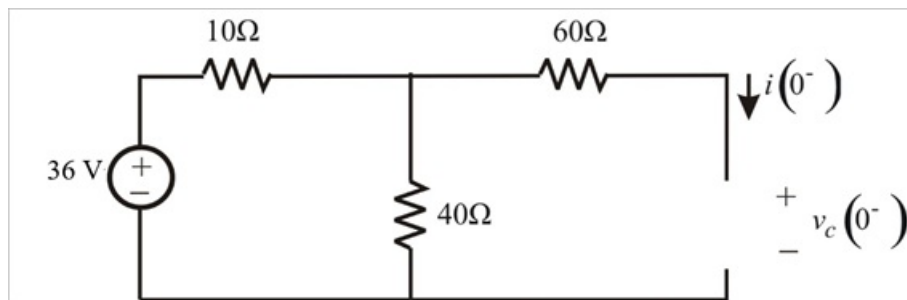


Figure 1

Step 2 of 5

Calculate the initial voltage across the capacitor using voltage division method.

$$\begin{aligned} v_c(0^-) &= 36 \left(\frac{40}{40 + 10} \right) \\ &= 36 \left(\frac{4}{5} \right) \\ &= 28.8 \text{ V} \end{aligned}$$

Since the circuit is open, the initial inductor current is $i(0^-) = 0 \text{ A}$.

In steady state, $i_L(0^-) = i_L(0^+) = i_L(0)$ and $v_c(0^-) = v_c(0^+) = v_c(0)$.

So,

$$\begin{aligned} i(0) &= 0 \text{ A} \\ v_c(0) &= 16 \text{ V} \end{aligned}$$

Step 3 of 5

Redraw the circuit for $t > 0$ in s-domain as shown in Figure 2.

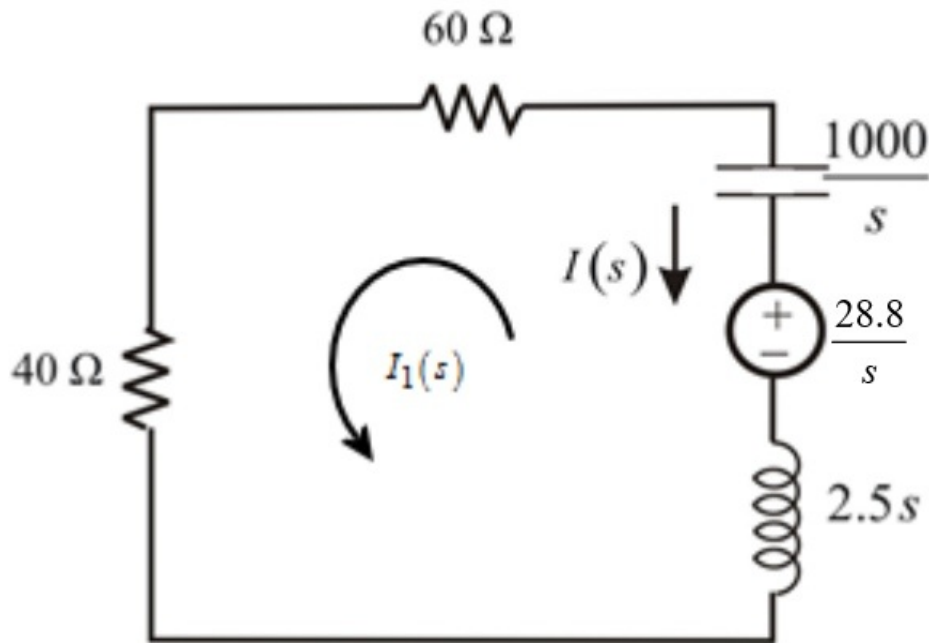


Figure 2

Step 4 of 5

Apply Kirchhoff's voltage law for the loop $I_1(s)$.

$$-\frac{28.8}{s} + 2.5sI_1(s) + \frac{1000}{s}I_1(s) + 40I_1(s) + 60I_1(s) = 0$$

$$I_1(s) \left[\frac{2.5s^2 + 1000 + 100s}{s} \right] = \frac{28.8}{s}$$

$$I_1(s) [s^2 + 40s + 400] = 11.52$$

$$I_1(s) = \frac{11.52}{s^2 + 40s + 400}$$

$$= \frac{11.52}{(s+20)^2}$$

Step 5 of 5

Apply inverse Laplace transform on both sides of equation $I_1(s)$.

$$i_1(t) = 11.52te^{-20t}u(t) \text{ A}$$

Calculate $i(t)$.

$$\begin{aligned} i(t) &= -i_1(t) \\ &= -11.52te^{-20t}u(t) \text{ A} \end{aligned}$$

Therefore, the current flowing through the inductor $i(t)$ is $-11.52te^{-20t}u(t) \text{ A}$.