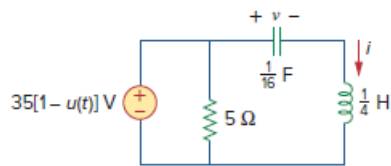


Problem

Calculate $i(t)$ for $t > 0$ in the circuit in Fig. 16.52.

Figure 16.52:



Step-by-step solution

Step 1 of 6

Refer to Figure 16.52 from the textbook.

The voltage source $35[1 - u(t)] = 35 \text{ V}$ for $t < 0$.

Consider that the circuit is in steady state for $t < 0$. The capacitor acts as an open circuit and the inductor acts as a short circuit in steady state.

Modify and redraw the circuit diagram for $t < 0$.

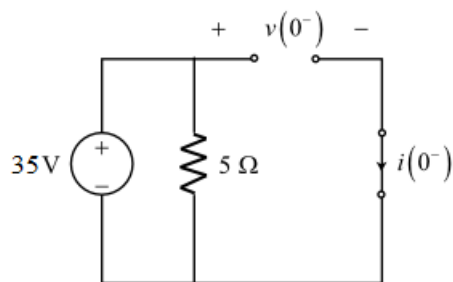


Figure 1

Step 2 of 6

Calculate the current $i(0^-)$ from the circuit in Figure 1.

$$i(0^-) = 0 \text{ A}$$

Inductor does not allow sudden changes in the current flowing through it. Therefore,

$$\begin{aligned} i(0^-) &= i(0^+) \\ &= i(0) \\ &= 0 \text{ A} \end{aligned}$$

Calculate the voltage $v(0^-)$ from the circuit in Figure 1.

$$v(0^-) = 35 \text{ V}$$

Capacitor does not allow sudden changes in the voltage across it. Therefore,

$$\begin{aligned} v(0^-) &= v(0^+) \\ &= v(0) \\ &= 35 \text{ V} \end{aligned}$$

Step 3 of 6

The voltage source $35[1-u(t)] = 0$ (short circuit) for $t > 0$.

Modify and redraw the circuit diagram for $t > 0$.

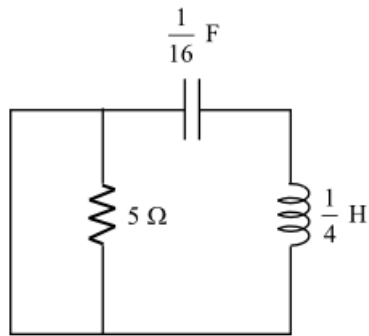


Figure 2

Step 4 of 6

Simplify the circuit in Figure 2.

$$R = 0$$

Represent the circuit in s-domain including the initial values.

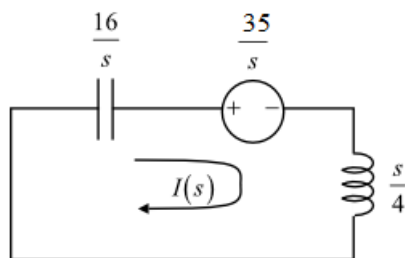


Figure 3

[Comments \(1\)](#)



Anonymous

why can we set $R=0$?

Step 5 of 6

Apply Kirchhoff's voltage law to the circuit in Figure 3.

$$\frac{16}{s} I(s) + \frac{35}{s} + \frac{s}{4} I(s) = 0$$

$$I(s) \left[\frac{16}{s} + \frac{s}{4} \right] = -\frac{35}{s}$$

$$I(s) \left[64 + s^2 \right] = -\frac{35}{s} (4s)$$

$$I(s) = \frac{-140}{s^2 + 8^2}$$

$$= -17.5 \left(\frac{8}{s^2 + 8^2} \right)$$

Step 6 of 6

Find the inverse Laplace transform to find the current $i(t)$.

Use the following properties of the Laplace transform:

$$\sin \omega t \leftrightarrow \frac{\omega}{s^2 + \omega^2}$$

Find the inverse Laplace transform of the function $I(s)$.

$$i(t) = -17.5 L^{-1} \left\{ \frac{8}{s^2 + 8^2} \right\}$$

$$i(t) = -17.5 \sin 8t u(t)$$

$$= 17.5 [-\sin 8t] u(t)$$

$$= 17.5 \cos(8t + 90^\circ) u(t) \text{ A}$$

Thus, the current $i(t)$ for $t > 0$ is $i(t) = 17.5 \cos(8t + 90^\circ) u(t) \text{ A}$.