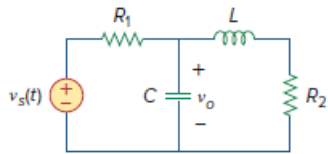


Problem

Using Fig. 16.56, design a problem to help other students understand how to use Thevenin's theorem (in the s -domain) to aid in circuit analysis.


Figure 16.56:



Step-by-step solution

Step 1 of 7

The circuit in s -domain

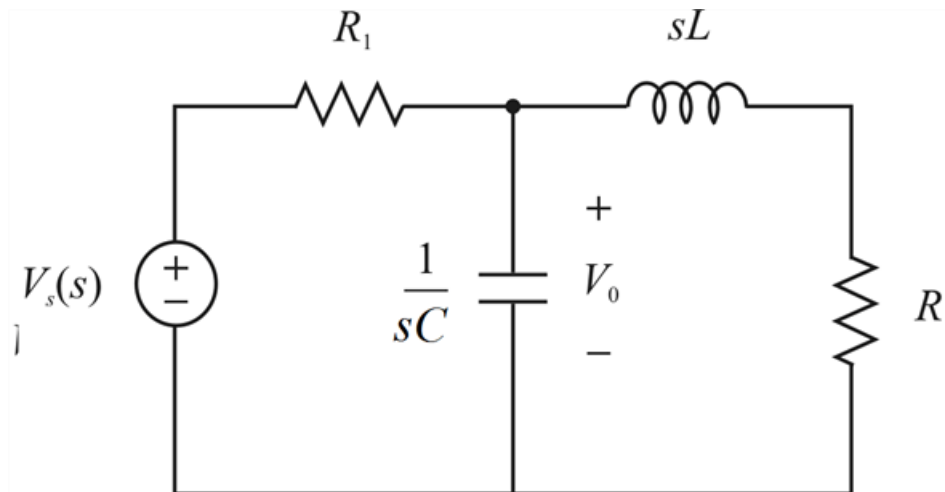


Step 2 of 7

$$i_L(0) = 0 \text{ zero for all } t < 0$$

$$v_C(0) = 0 \text{ for } t < 0$$

Step 3 of 7

For the Thevenin impedance

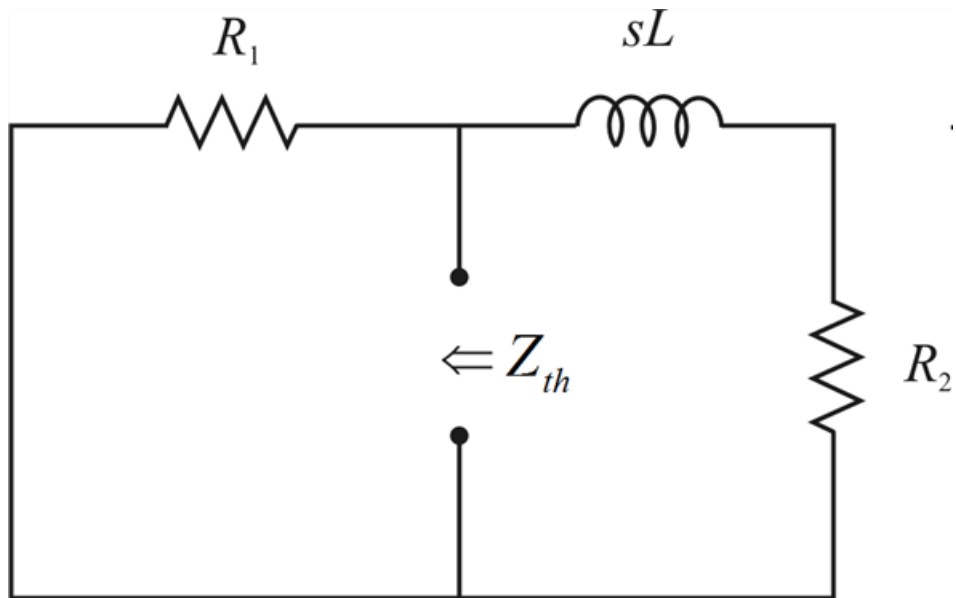

Step 4 of 7

sL inductor and R_2 resistor are in series and in parallel with R_1 resistor


$$Z_{th} = R_1 \parallel (sL + R_2)$$

$$Z_{th} = \frac{R_1 (sL + R_2)}{R_1 + R_2 + sL}$$

$$Z_{th} = \frac{R_1 \left(s + \frac{R_2}{L} \right)}{s + \left(\frac{R_1 + R_2}{L} \right)}$$

Step 5 of 7

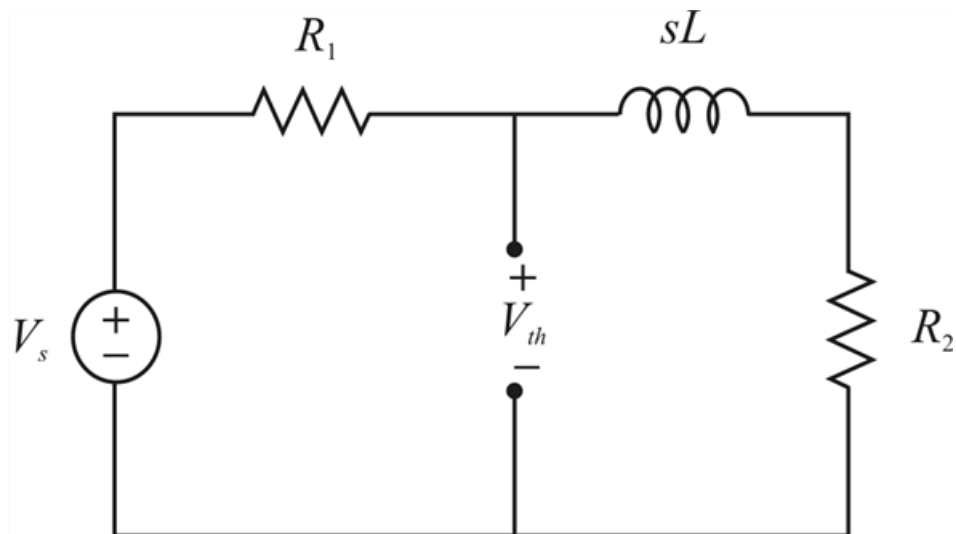Thus, the Thevenin voltage by the circuit



Step 6 of 7

Using nodal analysis, we get

$$\frac{V_{th} - V_s}{R_1} + \frac{V_{th}}{sL + R_2} = 0$$

$$V_{th} \left(\frac{1}{R_1} + \frac{1}{sL + R_2} \right) = \frac{V_s}{R_1}$$


$$V_{th} \left(\frac{sL + R_2 + R_1}{R_1 (sL + R_2)} \right) = \frac{V_s}{R_1}$$

$$V_{th} = \frac{V_s (sL + R_2)}{sL + R_2 + R_1}$$

$$V_{th} = \left[\frac{s + \frac{R_2}{L}}{s + \frac{R_1 + R_2}{L}} \right] V_s$$

Step 7 of 7

Thus, the Thevenin circuit is

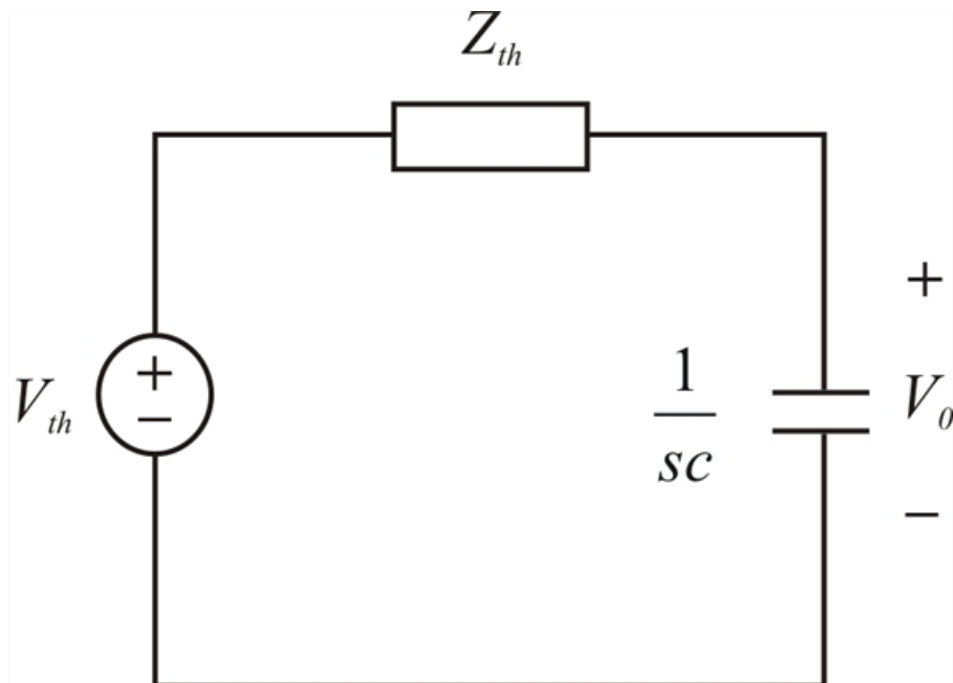

By the voltage division method,

$$V_o = \frac{\frac{1}{sC}}{\frac{1}{sC} + Z_{th}} V_{th}$$

$$V_o = \left[\frac{\frac{1}{sC}}{\frac{1}{sC} + \frac{R_1 \left(s + \frac{R_2}{L} \right)}{s + \frac{R_1 + R_2}{L}}} \right] \left[\frac{s + \frac{R_2}{L}}{s + \frac{R_1 + R_2}{L}} \right]$$

$$V_o = \left[\frac{s + \frac{R_1 + R_2}{L}}{s + \frac{R_1 + R_2}{L} + s^2 R_1 C + s \frac{R_2 R_1 C}{L}} \right] \left[\frac{s + \frac{R_2}{L}}{s + \frac{R_1 + R_2}{L}} \right]$$

$$V_o = \frac{s + \frac{R_2}{L}}{s^2 R_1 C + s \left(1 + \frac{R_1 R_2 C}{L} \right) + \left(\frac{R_1 + R_2}{L} \right)}$$

Assume the values and substitute in the expression and solve using partial fraction expansion, then by taking inverse transform we get the required output voltage $v_o(t)$.