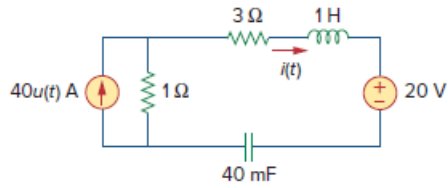


Problem

For the network in Fig. 16.62, find $i(t)$ for $t > 0$.

Figure 16.62:



Step-by-step solution

Step 1 of 5

Refer to circuit diagram in Figure 16.62 in the textbook.

It is known that,

$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t \geq 0 \end{cases}$$

For $t < 0$, the value of current source magnitude is zero. Capacitor acts as open circuit and inductor acts as short circuit.

The modified circuit is shown in Figure 1.

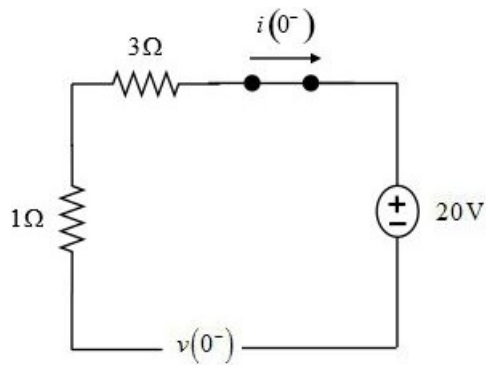


Figure 1

Step 2 of 5

The circuit is not a closed circuit, the current through the inductor is 0 A.

$$i(0^-) = 0 \text{ A}$$

The voltage across the capacitor for $t < 0$ is,

$$v(0^-) = 20 \text{ V}$$

Step 3 of 5

For $t > 0$, the s-domain circuit is shown in Figure 2.

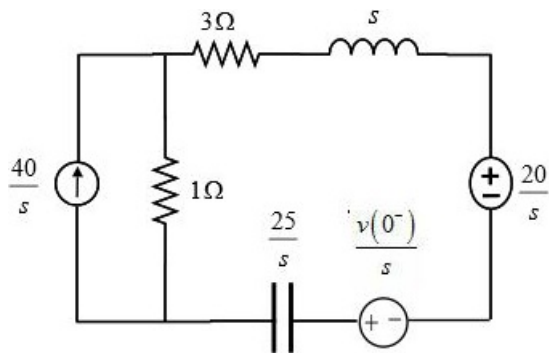


Figure 2

Step 4 of 5

Replace current source in parallel with resistance by an equivalent voltage source in series with the same resistance. The modified circuit is shown in Figure 3.

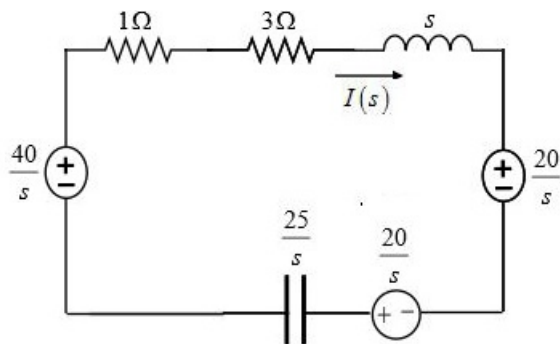


Figure 3

Step 5 of 5

Apply Kirchhoff voltage law.

$$-\frac{40}{s} + (1+3)I(s) + sI(s) + \frac{20}{s} - \frac{20}{s} + \frac{25}{s}I(s) = 0$$

$$I(s) \left[s + 4 + \frac{25}{s} \right] = \frac{40}{s}$$

$$I(s) [s^2 + 4s + 25] = 40$$

$$\begin{aligned} I(s) &= \frac{40}{s^2 + 4s + 25} \\ &= \frac{40}{(s+2)^2 + 21} \\ &= \frac{(8.733)(4.58)}{(s+2)^2 + 4.58^2} \end{aligned}$$

It is known that,

$$L^{-1} \left(\frac{b}{(s+a)^2 + b^2} \right) = e^{-at} \sin(bt) u(t)$$

Apply Inverse Laplace transform.

$$i(t) = 8.733e^{-2t} \sin(4.58t) \text{ A}$$

Therefore, the current, $i(t)$ for $t > 0$ is $\boxed{8.733e^{-2t} \sin(4.58t) \text{ A}}$.