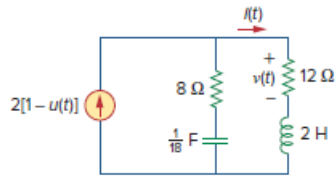


## Problem

Given the circuit shown in Fig. 16.75, determine the values for  $i(t)$  and  $v(t)$  for all  $t > 0$ .

**Figure 16.75:**



## Step-by-step solution

## Step 1 of 6

Refer to circuit diagram in Figure 16.75 in the textbook.

For  $t < 0$ , the circuit is in the steady state. Thus, the capacitor behave as an open circuit and the inductor behave as a short circuit.

The input current is  $2[1 - u(t)]$  A.

It is known that,

$$u(t) = \begin{cases} 1, & t > 0 \\ 0, & t < 0 \end{cases}$$

For  $t < 0$ , the value of input current is  $2$  A.

Redraw the circuit for  $t < 0$  as shown in Figure 1.

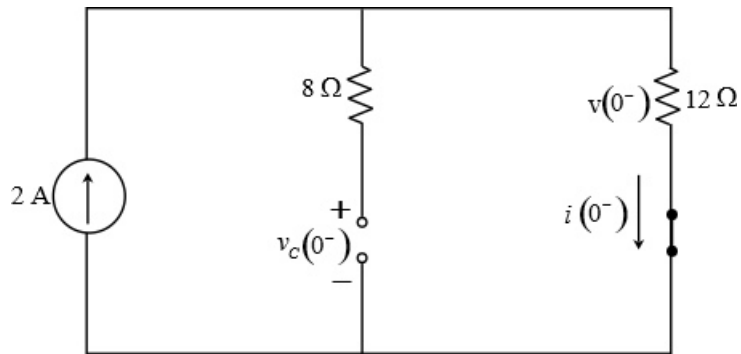


Figure 1

## Step 2 of 6

Calculate the initial current through the inductor.

$$i(0^-) = 2 \text{ A}$$

Calculate the voltage across  $12 \Omega$  resistor.

$$\begin{aligned} v(0^-) &= 12i(0^-) \\ &= (12)(2) \\ &= 24 \text{ V} \end{aligned}$$

Since the capacitor branch is open, the voltage across the capacitor is equal to the voltage  $v(0^-)$ , that is,

$$\begin{aligned} v_c(0^-) &= v(0^-) \\ &= 24 \text{ V} \end{aligned}$$

### Step 3 of 6

For  $t > 0$ , calculate the value of input current.

$$\begin{aligned} I(t) &= 2[1 - u(t)] \\ &= 2(1 - 1) \\ &= 0 \text{ A} \end{aligned}$$

Since the value of input current is  $0 \text{ A}$  for  $t > 0$ , the input branch is open.

Redraw the circuit for  $t > 0$  in s-domain as shown in Figure 2.

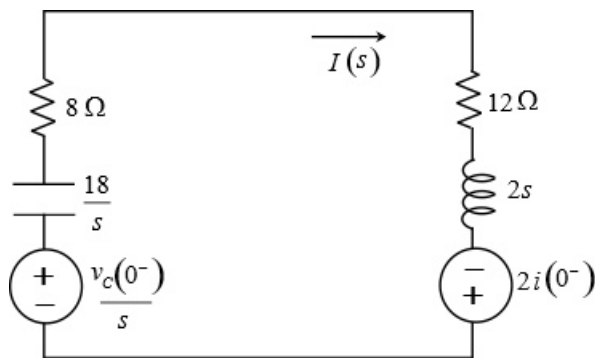


Figure 2

### Step 4 of 6

Apply Kirchhoff's voltage law in the loop.

$$-\frac{v_c(0^-)}{s} + I(s) \left( \frac{18}{s} + 8 + 12 + 2s \right) - 2i(0^-) = 0$$

Substitute  $24 \text{ V}$  for  $v_c(0^-)$  and  $2 \text{ A}$  for  $i(0^-)$ .

$$I(s) \left( 2s + 20 + \frac{18}{s} \right) = \frac{24}{s} + 2(2)$$

$$I(s) \left( \frac{2s^2 + 20s + 18}{s} \right) = \frac{24 + 4s}{s}$$

$$\begin{aligned} I(s) &= \frac{2s + 12}{s^2 + 10s + 9} \\ &= \frac{2(s + 6)}{(s + 1)(s + 9)} \end{aligned}$$

### Step 5 of 6

Convert  $\frac{s+6}{(s+9)(s+1)}$  into its partial fraction form.

$$\begin{aligned}\frac{s+6}{(s+9)(s+1)} &= \frac{A}{s+9} + \frac{B}{s+1} \\ &= \frac{A(s+1)+B(s+9)}{(s+9)(s+1)}\end{aligned}$$

Compare the coefficients of  $s$  and the constant terms on both the sides.

$$A+B=1 \dots\dots (1)$$

$$A+9B=6 \dots\dots (2)$$

Solve equation (1) and equation (2).

$$A=0.375$$

$$B=0.625$$

The partial fraction form of  $\frac{s+6}{(s+9)(s+1)}$  is  $\frac{0.375}{s+9} + \frac{0.625}{s+1}$ .

#### Step 6 of 6

The current expression is,

$$\begin{aligned}I(s) &= 2\left(\frac{0.375}{s+9} + \frac{0.625}{s+1}\right) \\ &= \frac{0.75}{s+9} + \frac{1.25}{s+1}\end{aligned}$$

Apply inverse Laplace transform.

$$\begin{aligned}i(t) &= \mathcal{L}^{-1}\left[\frac{0.75}{s+9}\right] + \mathcal{L}^{-1}\left[\frac{1.25}{s+1}\right] \\ &= 0.75e^{-9t}u(t) + 1.25e^{-t}u(t) \\ &= [0.75e^{-9t} + 1.25e^{-t}]u(t) \text{ A}\end{aligned}$$

Therefore, the value of  $i(t)$  is  $\boxed{[0.75e^{-9t} + 1.25e^{-t}]u(t) \text{ A}}$ .