


Problem

In the circuit of Fig. 16.76, the switch has been in position 1 for a long time but moved to position 2 at $t = 0$. Find:

(a) $v(0^+)$, $dv(0^+)/dt$

(b) $v(t)$ for $t \geq 0$.

Figure 16.76:

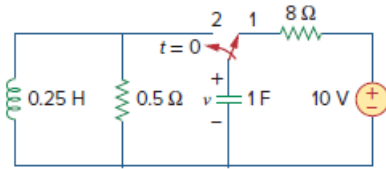

Step-by-step solution

Step 1 of 7

(a)

Refer to Figure 16.76 in the textbook.

At $t < 0$, the switch has been in position 1 for a long time. Thus, the circuit was in steady state before $t = 0$.

An inductor behaves as a short circuit and a capacitor behaves as an open circuit in steady state.

Redraw the Figure for $t < 0$ as shown in Figure 1.

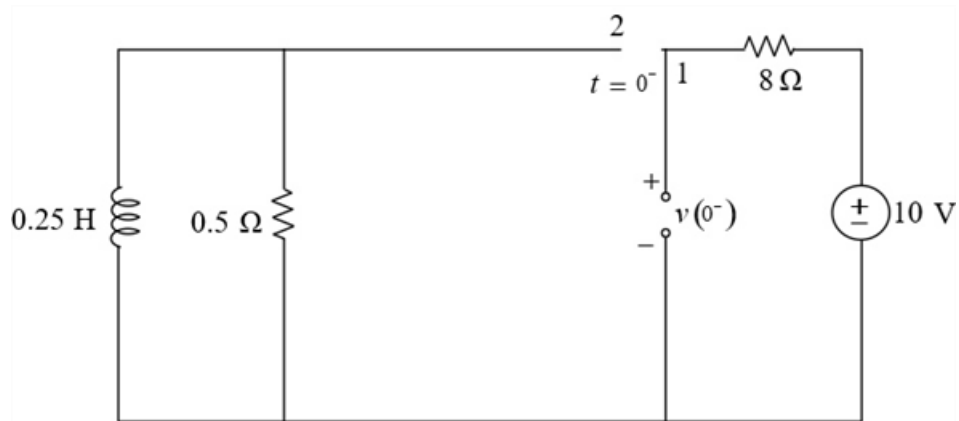


Figure 1

Step 2 of 7

The initial current through the inductor is zero.

$$i_L(0^-) = 0 \text{ A}$$

Calculate the initial voltage across the capacitor.

$$10 - 8(i) - v(0^-) = 0$$

$$10 - 8(0) - v(0^-) = 0$$

$$v(0^-) = 10 \text{ V}$$

Capacitor does not allow sudden change in the voltage, that is,

$$v(0^+) = v(0^-)$$

Substitute 10 V for $v(0^-)$.

$$v(0^+) = 10 \text{ V}$$

Hence, the value of $v(0^+)$ is $\boxed{10 \text{ V}}$.

Step 3 of 7

Redraw the circuit in Figure 1 for the switch in position 2 as shown in Figure 2.

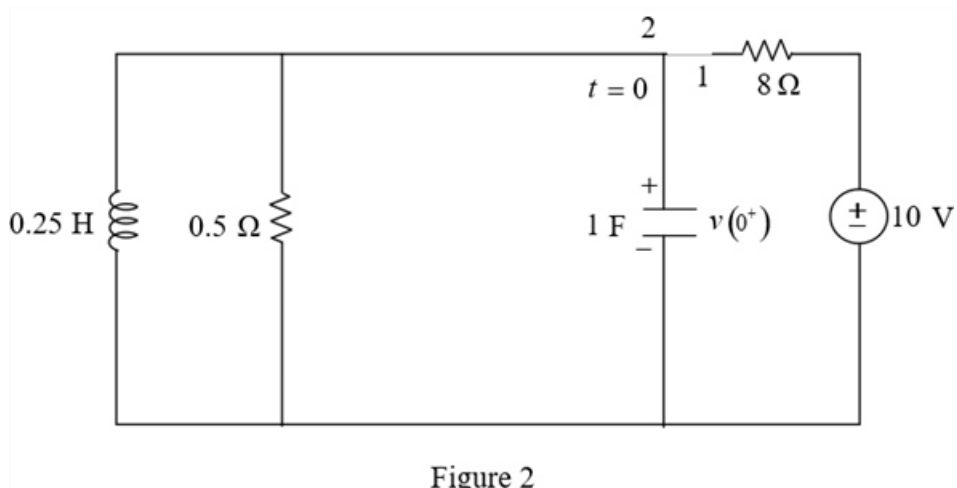


Figure 2

Step 4 of 7

Apply Kirchhoff's Current Law in Figure 2.

$$1 \frac{dv(0^+)}{dt} + \frac{v(0^+)}{0.5} + i_L(0^+) = 0$$

Substitute 10 V for $v(0^+)$ and 0 A for $i_L(0^+)$.

$$1 \frac{dv(0^+)}{dt} + \frac{10}{0.5} + 0 = 0$$

$$\frac{dv(0^+)}{dt} = -20 \text{ V/s}$$

Hence, the value of $\frac{dv(0^+)}{dt}$ is $\boxed{-20 \text{ V/s}}$.

Step 5 of 7

(b)

Redraw the circuit in Figure 2 in s-domain as shown in Figure 3.

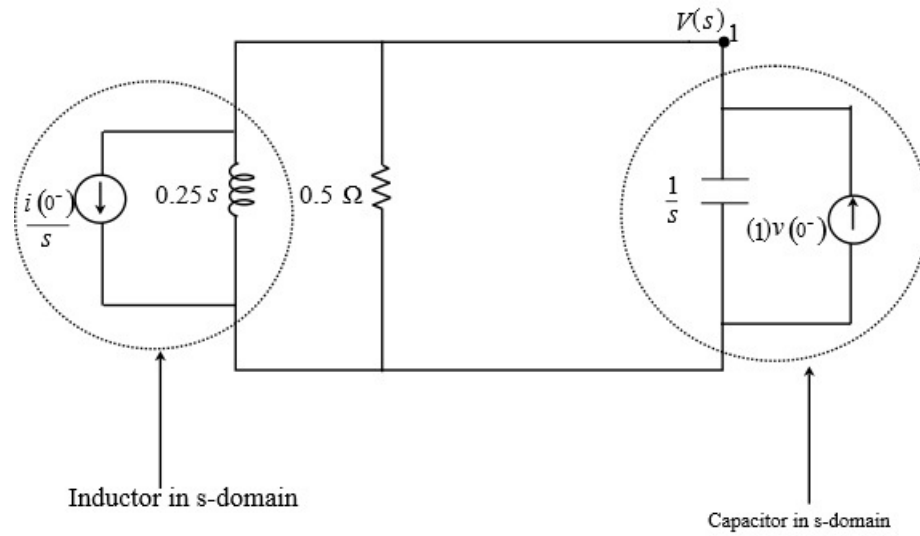


Figure 3

Step 6 of 7

Apply Kirchhoff's Current Law at node 1.

$$\frac{V(s)}{\left(\frac{1}{s}\right)} - v(0^-) + \frac{V(s)}{0.5} + \frac{V(s)}{0.25s} + \frac{i(0^-)}{s} = 0$$

Substitute 10 V for $v(0^-)$ and 0 A for $i(0^-)$.

$$sV(s) - 10 + 2V(s) + 4\frac{V(s)}{s} = 0$$

$$\left(s + 2 + \frac{4}{s}\right)V(s) = 10$$

$$\left(\frac{s^2 + 2s + 4}{s}\right)V(s) = 10$$

$$V(s) = \frac{10s}{s^2 + 2s + 4}$$

$$= \frac{10s}{(s+1)^2 + (\sqrt{3})^2}$$

$$= \frac{10(s+1) - 10}{(s+1)^2 + (\sqrt{3})^2}$$

$$= \frac{10(s+1)}{(s+1)^2 + (\sqrt{3})^2} - \frac{5.773\sqrt{3}}{(s+1)^2 + (\sqrt{3})^2}$$

Step 7 of 7

Apply inverse Laplace transform.

$$\begin{aligned} v(t) &= 10\mathcal{L}^{-1}\left[\frac{(s+1)}{(s+1)^2+(\sqrt{3})^2}\right] - 5.773\mathcal{L}^{-1}\left[\frac{\sqrt{3}}{(s+1)^2+(\sqrt{3})^2}\right] \\ &= 10e^{-t}\cos(1.732t)u(t) - 5.773e^{-t}\sin(1.732t)u(t) \\ &= e^{-t}[10\cos(1.732t) - 5.773\sin(1.732t)]u(t) \text{ V} \end{aligned}$$

Consider $10 = r \cos \theta$ and $5.77 = r \sin \theta$.

$$r^2 \cos^2 \theta + r^2 \sin^2 \theta = 10^2 + 5.77^2$$

$$r^2 = 132.49$$

$$r = 11.5$$

$$\frac{r \sin \theta}{r \cos \theta} = \frac{5.77}{10}$$

$$\tan \theta = 0.577$$

$$\theta = 30^\circ$$

Substitute $11.5 \cos 30^\circ$ for 10 and $11.5 \sin 30^\circ$ for 5.77 in the voltage expression.

$$\begin{aligned} v(t) &= e^{-t}[11.5 \cos(30^\circ) \cos(1.732t) - 11.5 \sin(30^\circ) \sin(1.732t)] \\ &= 11.5e^{-t}[\cos(30^\circ) \cos(1.732t) - \sin(30^\circ) \sin(1.732t)] \\ &= 11.5e^{-t} \cos(1.732t + 30^\circ) \text{ V} \end{aligned}$$

Therefore, the value of voltage $v(t)$ is $\boxed{[11.5e^{-t} \cos(1.732t + 30^\circ)] \text{ V}}$.